



സി.പി.എഫ്

SFI GEC PALAKKAD

MODULE - 3

AC CIRCUIT

$$(-1) 10 + j 30$$

(1) Add two voltages $50 \angle 30^\circ$ and $30 \angle -45^\circ$ and show the result in polar form.

Ans: $\begin{array}{l} 50 \angle 30^\circ \\ \downarrow \\ 43.30 + j 25 \end{array} \quad \begin{array}{l} 30 \angle -45^\circ \\ \rightarrow \\ 21.21 - j 21.21 \end{array}$

$$= 64.51 + j 3.79$$

$$= 64.62 \angle 3.36^\circ$$

(2) Perform the following operation and give the result in polar form.

$$\begin{array}{l} (10 - j 10) (10 \angle -60^\circ) (10 e^{j 30}) \\ \downarrow \\ (14.14 \angle -45^\circ) (10 \angle -60^\circ) (10 \angle 30^\circ) \end{array}$$

$$\underline{\underline{14.14 \angle -75}}$$


$$(3) \frac{(5 e^{j 30}) (2 - j 4)}{(3 + j 3) (2 \angle -15)}$$

Ans: $\frac{(5 \angle 30) (4.47 \angle -63.43)}{(4.24 \angle 45) (2 \angle -15)} = \frac{(22.35 \angle -33.43)}{(8.48 \angle 30)}$


$$= (2.63 \angle -63.43)$$

AC Circuits Phasor diagram

Circuit with resistance

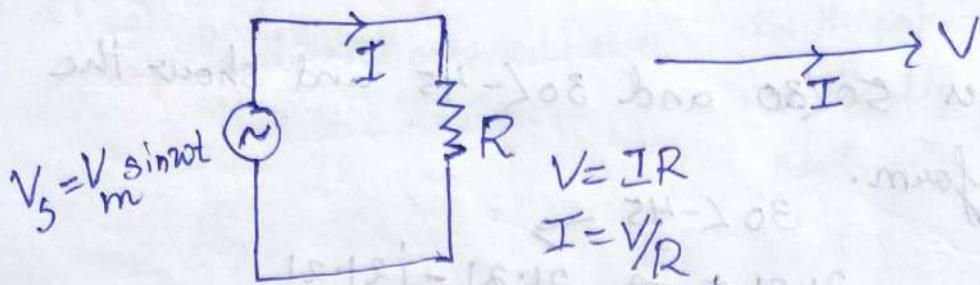

Circuit with inductor

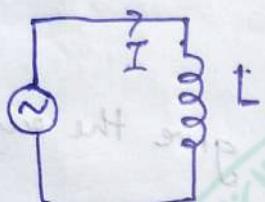

~~$e = L \frac{dI}{dt}$, voltage the arrow the inductor~~

~~$V_m \sin \omega t = L \frac{di}{dt}$~~

~~$V_m \sin \omega t dt = L dI$~~

~~$\int \frac{V_m}{L} \sin \omega t dt = \int dI$~~

~~$I = \frac{V_m}{L} \int \sin \omega t dt$~~

~~$I = \frac{V_m}{L \omega} - \cos \omega t$~~

~~$I = \frac{V_m}{(L \omega)} - \cos \omega t$~~


$\text{Law} = X_L$, inductive reactance.

$\omega = 2\pi f$ (angular frequency)

$$I = V_m - (\cos \omega t)$$

$$I = I_m \sin(\omega t - \pi/2)$$

$$V_s = \underline{V_m \sin \omega t}$$

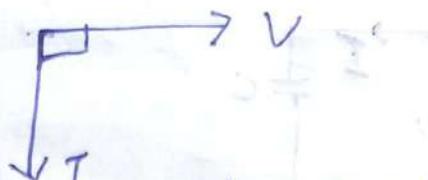

Current lags by phase of 90° behind voltage.

Power in Purely inductive circuit

$$P = VI$$

$$= V_m \sin \omega t \cdot I_m \cos \omega t$$

$$= -V_m I_m \sin \omega t \cos \omega t$$

$$= -V_m I_m \frac{\sin 2\omega t}{2}$$

$$= -\frac{V_m I_m}{2} \sin 2\omega t$$

$$\text{Average power} = \frac{1}{2\pi} \int_0^{2\pi} -\frac{V_m I_m}{2} \sin 2\omega t d\omega t$$

$$= -\frac{V_m I_m}{4\pi} \int_0^{2\pi} \sin 2\omega t d\omega t$$

$$= -\frac{V_m I_m}{4\pi} \left[-\frac{\cos 2\omega t}{2} \right]_0^{2\pi}$$

$$= -\frac{V_m I_m}{8\pi} \left[-\cos 4\pi - (-\cos 0) \right]$$

$$= -\frac{V_m I_m}{8\pi} \left[-1 + 1 \right] = 0$$

Average Power in purely inductive circuit is zero.

$$\nabla V_m \sin \omega t = L dI/dt$$

$$V_m \sin \omega t dt = L dI$$


$$\int V_m \sin \omega t dt = \int L dI$$

$$I = \frac{V_m}{L} (\sin \omega t + C)$$

$$I = \frac{V_m \cos \omega t}{L \omega}$$

$$I = I_m \sin(\omega t - \pi/2)$$

Circuit with capacitance

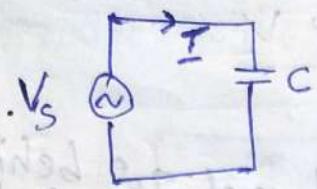

$$i = \frac{dq}{dt}$$

$$q = CV$$

$$i = \frac{d(CV)}{dt}$$

$$i = C \frac{dv}{dt}$$

$$i = C \frac{d}{dt} V_m \sin \omega t$$

$$i = C V_m \frac{d}{dt} \sin \omega t$$

$$i = C V_m \cos \omega t \cdot \omega$$


$$i = C V_m \omega \cos \omega t$$

$$i = \frac{V_m}{1/C\omega} \sin(\omega t + 90^\circ)$$

$$i = \frac{V_m}{X_C} \sin(\omega t + 90^\circ)$$

$$i = I_m \sin(\omega t + 90^\circ)$$

$$V = V_m \sin \omega t$$

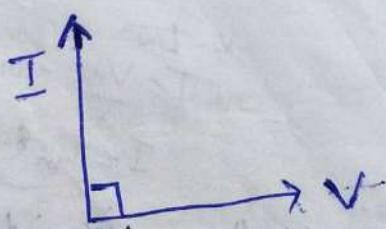

$$(I_{max}) = \frac{V_m}{X_C}$$

Power in Purely ~~inductive~~ capacitive Circuit

$$P = V \cdot I$$

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t + 90^\circ)$$

$$= V_m I_m \sin \omega t \cdot \cos \omega t$$

$$= V_m I_m \frac{\sin 2\omega t}{2}$$

$$= \frac{V_m \cdot I_m}{2} \cdot \sin 2\omega t$$

$$\text{Average power} = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m \cdot I_m}{2} \sin 2\omega t d\omega t$$


$$= \frac{V_m I_m}{4\pi} \int_0^{2\pi} \sin 2\omega t d\omega t$$

$$= \frac{V_m I_m}{4\pi} \left[\frac{-\cos 2\omega t}{2} \right]_0^{2\pi}$$

$$= \frac{V_m I_m}{8\pi} \left[-\cos 2\pi + \cos 0 \right]$$

~~$$\text{Average power} = \frac{V_m I_m \times 0}{8\pi} = 0\%$$~~

Series RL circuit

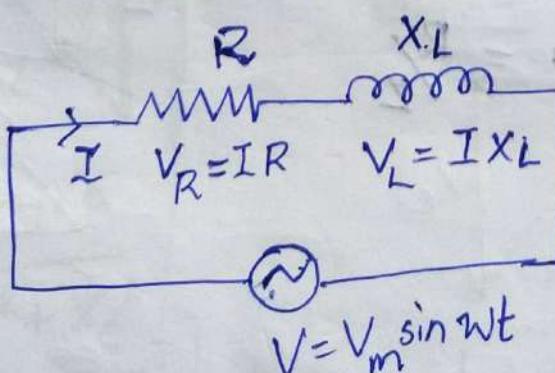

$$\text{Given } V = IR \rightarrow V = Ix_L \rightarrow \text{Voltage drop}$$


$$V = \sqrt{V_R^2 + V_L^2} = \sqrt{(IR)^2 + (Ix_L)^2}$$

$$V = I\sqrt{R^2 + X_L^2}$$

Impedance unit Ω

$$Z = \sqrt{R^2 + X_L^2}$$

$$V = IZ$$

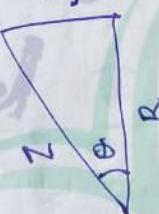

\rightarrow Impedance Δ e


$$|Z| = \sqrt{R^2 + X_L^2} \rightarrow \text{Magnitude}$$

$$Z = R + jX_L \rightarrow \text{Rectangular form}$$

Power factor, $\cos \theta = R/Z$


$$X_L = L\omega \quad \text{where } \omega = 2\pi f$$

RC Circuit

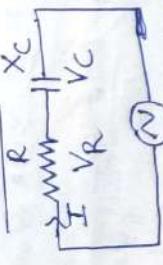

$$V_s = V_m \sin \omega t$$

$$I = \frac{V_s}{R + jX_C}$$

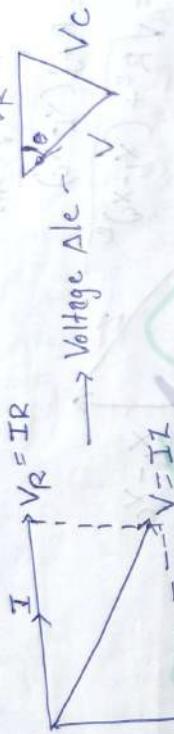


$$V = \sqrt{V_R^2 + V_C^2}$$

$$V = \sqrt{I^2 R^2 + I^2 X_C^2}$$

$$V = I \sqrt{R^2 + X_C^2}$$

$$V = I Z, \text{ where } Z = \sqrt{R^2 + X_C^2}$$

Impedance Alc

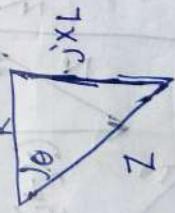

$$Z = R - jX_L$$

$$Z = \sqrt{R^2 + X_C^2}$$

$X_C = \text{Capacitive reactance } X_C = \frac{1}{\omega C}$

Voltage Alc $\rightarrow V = I Z$

GEO


Unit of impedance = Ohm

$V = I Z$

Unit

of


impedance

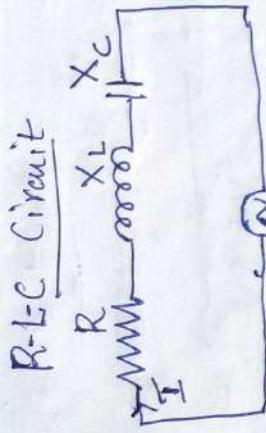

$$V = V_m \sin \omega t$$

$$Z = R + j(X_L - X_C)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

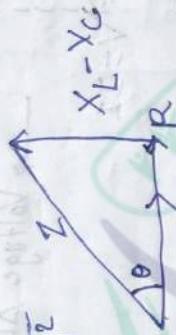

R-L Circuit

• Impedance $Z = R + jX_L$

$$Z = \sqrt{R^2 + X_L^2}$$


$$X_L = L \cdot 2\pi f$$

$$I = \frac{V}{Z}$$

• Current $I = V/Z$

Power factor $\cos \theta = R/Z$

Impedance angle

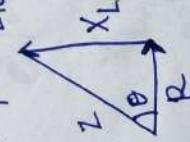

R-C Circuit

• Impedance $Z = R - jX_C$



$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$X_C = \frac{1}{C \cdot 2\pi f}$$

$$I = \frac{V}{Z}$$

$$= \frac{1}{C \cdot 2\pi f}$$

Impedance angle

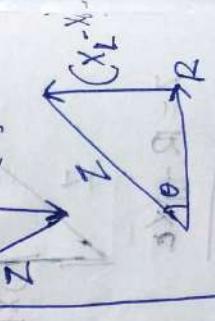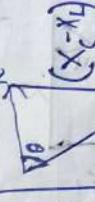

power factor $\cos \theta = R/Z$



R-L-C Circuit

$$Z = R + j(X_L - X_C)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$I = \frac{V}{Z}$$

Impedance angle

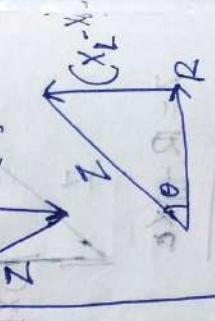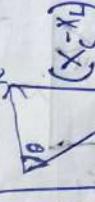

power factor $\cos \theta = R/Z$

Q) A resistor of 50 ohm and an inductor of 0.1 H are connected in series across a 200V, 50Hz supply. Find the



- (i) Impedance
- (ii) Power factor
- (iii) Active power
- (iv) Reactive power

$$\text{Ans: } R = 50\Omega$$

~~$$L = 0.1\text{H}$$~~

~~$$V = 200\text{V}$$~~

~~$$f = 50\text{Hz}$$~~

$$I = V/Z$$

$$= \frac{200}{59.05} = \underline{\underline{3.386\text{A}}}$$

~~$$\omega = 2\pi f = 2\pi \times 50 = \underline{\underline{314.159}}$$~~

~~$$X_L = L\omega = 0.1 \times 314.159 = \underline{\underline{31.42\Omega}}$$~~

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{(50)^2 + (31.42)^2} = \underline{\underline{59.05\Omega}}$$

(i) Power factor, $\cos\theta = R/Z$

$$\cos\theta = \frac{50}{59.05} = \underline{\underline{0.846}}$$

(ii) Active power, $P = VI \cos\theta = 200 \times 3.386 \times 0.846$

$$= \underline{\underline{572.91\text{W}}}$$

(iii) Reactive power, $Q = VI \sin\theta = 200 \times 3.386 \times 0.532$

$$= \underline{\underline{360.27\text{VAR}}}$$


$$\left(\sin\theta = \frac{X_L}{Z} \right) = 0.532$$

Power & Energy

written

- ① Active power, ~~It is~~ $P = VI \cos \theta$ Unit Watt WATT
- ② Reactive power $Q = VI \sin \theta$ Unit Volt Amper Reactive VAR or KVAR
- ③ Apparent power $S = VI$ Unit Volt Ampere VA or KVA

~~This is actual power~~

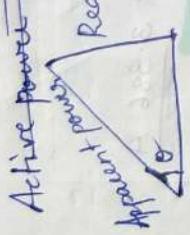

Active power

$$\cos \theta = \frac{\text{Active power}}{\text{Apparent power}}$$

- Active power (P) ~~It is~~ is the actual power dissipated in the circuit

- Reactive power (Q) - It is the power associated with the reactive components. (Inductance and Capacitance of the circuit)
- Reactive power is not dissipated in circuit but stored
- It is also called wattless component of power. $Q = VI \sin \theta$

$$P = VI \cos \theta \quad \text{Unit} = \text{WATT}$$

Volt Amper Reactive.

- Apparent power (S) - It is the product of R.M.S Voltage and current in the circuit

$$S = VI \quad \text{Unit} = \text{VA or KVA}$$

$$S = \sqrt{P^2 + Q^2}$$

- Power factor $\cos \theta$ is defined as the ratio of active power by apparent power. From the impedance $\cos \theta$, it is also

written as $\cos \theta = R/Z$

2) A resistor of $50\ \Omega$ and a capacitor of $100\ \mu F$ are connected in series across a $100V, 50\ Hz$ supply. Find

(i) Impedance

(ii) Current

(iii) Power factor

(iv) Voltage across resistor.

(v) Voltage across capacitor.

(vi)



$$X_C = \frac{1}{C\omega} = \frac{1}{100 \times 10^{-6} \times 2\pi \times 50}$$

$$= \underline{31.83\ \Omega}$$

$$\text{Ans: (i)} Z = \sqrt{R^2 + X_C^2} = \underline{\underline{59.27\ \Omega}}$$

$$\text{(ii)} I = \underline{\underline{V/Z}} = \underline{\underline{\frac{100}{59.27}}} = \underline{\underline{1.687\ A}}$$

$$\text{(iii)} \text{Power factor, } \cos \theta = \underline{\underline{R/Z}} = \underline{\underline{\frac{50}{59.27}}} = \underline{\underline{0.843}}$$

-)

(iv) Voltage across resistor, $V = IR$


$$\text{Ans: } V = \underline{\underline{I \times Z}} = \underline{\underline{1.687 \times 59.27}} = \underline{\underline{94.35\ V}}$$

arg

$$\text{(v) Voltage across capacitor, } V = \underline{\underline{I \times X_C}} = \underline{\underline{1.687 \times 31.83}} = \underline{\underline{53.69\ V}}$$

(vi) Voltage across $50\ \Omega$ resistor due to capacitor is

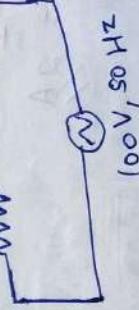3) A resistor of $0.1\ H$ and a capacitor of $400\ \mu F$ are connected in series and the combination is connected across a $100V, 50\ Hz$ supply. Find



(i) Power consumed

(ii) Power factor.

$$X_L = L\omega$$

$$X_C = \frac{1}{C\omega} = \frac{1}{40 \times 10^{-6} \times 2\pi \times 50} = \frac{31.42 \Omega}{= 79.6 \Omega}$$

~~$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (X_L - X_C)^2} = 55.$$~~

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \frac{69.4 \Omega}{= 69.4}$$

$$I = \frac{V_L}{Z} = \frac{100}{69.4} = 1.44 A$$

$$\text{Power factor } \cos \theta = \frac{R}{Z} = \frac{50}{69.4} = 0.72$$

$$P = V I \cos \theta = 100 \times 1.44 \times 0.72 = \underline{\underline{103.7 W}}$$

W if power factor lagging
A series RL circuit takes 160 W at 0.8 power factor lagging
from 100V, 50 Hz supply. What are the values of R and L?



Ans:

$$V_s = V_m \sin \omega t = 100V, 50 \text{ Hz}$$

$$\cos \theta = 0.8$$

$$P = 160 \text{ W}$$

$$P = V I \cos \theta$$

$$160 = 100 \times I \times 0.8$$

$$160 = 80 I$$

$$I = \frac{160}{80} = 2 A$$

$$V = IZ$$

~~$$Z = \frac{V}{I} = \frac{100}{2} = 50 \Omega$$~~

~~$$\cos \theta = R/Z$$~~

$$0.8 = \frac{R}{50}$$

$$R = 0.8 \times 50 = 40 \Omega$$

$$Z = \sqrt{R^2 + X_L^2}$$

~~$$Z = \sqrt{40^2 + X_L^2}$$~~

$$Z^2 = R^2 + X_L^2$$

$$X_L^2 = Z^2 - R^2$$

$$X_L^2 = \sqrt{Z^2 - R^2} = \sqrt{50^2 - 40^2} = 30 \Omega$$

$$X_L = L\omega$$

~~$$X_L = \frac{X_L}{\omega}$$~~

$$L = \frac{30}{2\pi \times 50} = 0.095 H$$

~~$$L = \frac{30}{2\pi \times 50} = 0.095 H \rightarrow 95.5 mH$$~~

Q) A 50 Hz sinusoidal voltage $40 + j30$ is applied across a series RL circuit resulting in ~~at~~ sinusoidal current $4 + j1 A$. Calculate

- (i) The impedance of the circuit
- (ii) Power consumed in the circuit
- (iii) Power factor of the circuit



$$V_s = V_m \sin \omega t$$

$$I = 4 + j1$$

$$V = 40 + j30 = 50 \angle 36.86^\circ = 4.12 \angle 14.03^\circ$$

$$(i) Z = \frac{V}{I} = \frac{50 \angle 36.86}{4.12 \angle 14.03} = 12.13 \angle 22.83$$

$$\begin{aligned} (ii) P &= VI \cos \theta \\ P &= 50 \times 4.12 \times \cos 22.83 \\ &= 189.86 \text{ W} \end{aligned}$$

$$(iii) \text{Power factor, } \cos \theta = \cos 22.83 = 0.921$$

- (6) A ~~230V~~ A ~~230V~~, 50 Hz supply is applied to a coil of resistance 10Ω and inductance 0.2 H . Calculate
 (i) the reactance and impedance of the coil
 (ii) current and its phase angle relative to applied voltage.



$$\begin{aligned} (i) X_L &= L \omega \\ X_L &= 0.2 \times 2\pi \times 50 = \frac{62.83 \Omega}{\sqrt{R^2 + X_L^2}} \\ Z &= \sqrt{R^2 + X_L^2} = \sqrt{10^2 + 62.83^2} = 63.62 \Omega \end{aligned}$$

$$(ii) V = IZ \\ I = \frac{V}{Z} = \frac{230}{63.62} = \frac{3.62 \text{ A}}{\text{A}}$$

$$\begin{aligned} (iii) \cos \theta &= R/Z = \frac{10}{63.62} = 0.154 \\ \theta &= \cos^{-1} 0.154 = \frac{80.96^\circ}{\text{A}} \end{aligned}$$

- (7) A series RLC circuit with a resistance of 50Ω , a capacitance of $25\mu F$ and an inductance of $0.15H$ is connected across $230V, 50Hz$ supply. Determine the impedance of the circuit.



$$X_L = L\omega$$

$$= 0.15 \times 2 \times \pi \times 50 = 47.12 \Omega$$

$$X_C = \frac{1}{C\omega} = \frac{1}{25 \times 10^{-6} \times 2 \times \pi \times 50} = 127.32 \Omega$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2} = \sqrt{50^2 + (127.32 - 47.12)^2} = 94.57 \Omega$$

(8) An alternating voltage $160+j120$ V is applied to a circuit when the current in the circuit is found to be

- 6+j8. Find
 (i) Impedance of the circuit
 (ii) Phase angle
 (iii) Power consumed

$$V = 160 + j120 = 200 \angle 36.86^\circ$$

$$I = 6 + j8 = 10 \angle 53.13^\circ$$

$$Z = \frac{V}{I} = \frac{200 \angle 36.86^\circ}{10 \angle 53.13^\circ} = 20 \angle -16.27 \Omega$$

$$(i) P = VI \cos \theta$$


$$= 200 \times 10 \times \cos 16.27^\circ = 1919.9 \text{ W}$$

$$(ii) \theta = \underline{\underline{16.27}}$$

(*)

Remedial

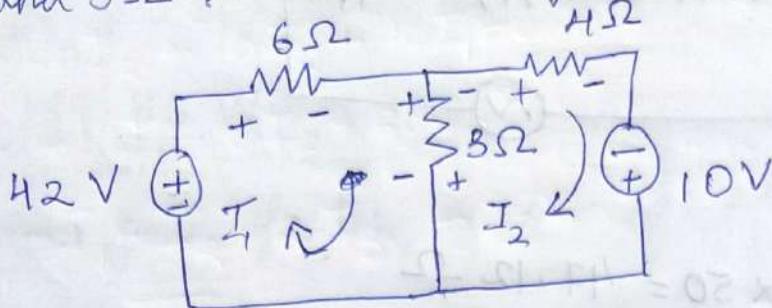- i) By mesh analysis, find the currents flowing through 4Ω and 3Ω resistors in the following network



Loop - 1

$$42 - 6I_1 - 3(I_1 - I_2) = 0$$

$$42 - 6I_1 - 3I_1 + 3I_2 = 0$$

$$42 - 9I_1 + 3I_2 = 0$$

$$42 = 9I_1 - 3I_2$$

$$14 = 3I_1 - I_2 \quad \text{--- ①}$$

Loop - 2

$$10 - 3(I_2 - I_1) - 4I_2 = 0$$

$$10 - 3I_2 + 3I_1 - 4I_2 = 0$$

$$10 - 7I_2 + 3I_1 = 0$$

$$10 = 7I_2 - 3I_1 \quad \text{--- ②}$$

$$14 = 3I_1 - I_2$$

$$3I_1 - I_2 = 14 \quad \times (1)$$

$$-3I_1 + 7I_2 = 10 \quad \times (3)$$

$$-8I_2 + I_2 = -14$$

$$(+) \quad 3I_1 - I_2 = 14$$

$$-3I_1 + 7I_2 = 10$$

$$\frac{0}{0} \quad 6I_2 = 24$$

$$I_2 = \frac{24}{6} = 4 \text{ A}$$

$$3I_1 - 4 = 14$$

$$3I_1 = 18$$


$$I_1 = \frac{18}{3} = \underline{\underline{6A}}$$

Current through 4Ω resistor = $I_2 = 4A$

Current through 3Ω resistor = $(I_1 - I_2) = 6 - 4 = \underline{\underline{2A}}$

Current through 6Ω resistor = $I_1 = \underline{\underline{6A}}$

2)

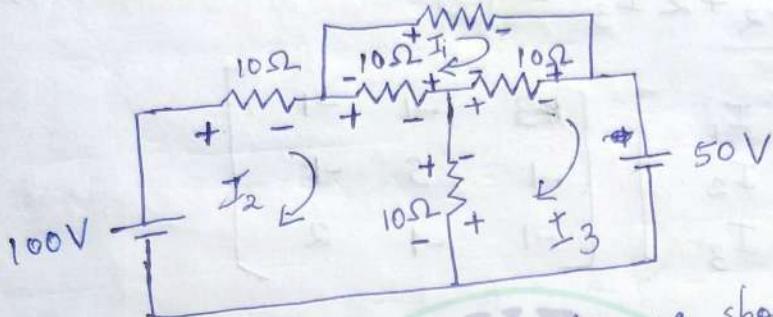

Find the mesh current in the figure shown by mesh analysis.

Loop - 1

$$-10I_1 - 10(I_1 - I_3) - 10(I_1 - I_2) = 0$$

$$-10I_1 - 10I_1 + 10I_3 - 10I_1 + 10I_2 = 0$$

$$-30I_1 + 10I_2 + 10I_3 = 0$$

$$0 = 30I_1 - 10I_2 - 10I_3$$

$$0 = \underline{\underline{3I_1 - I_2 - I_3}} - \textcircled{1}$$

-10 - 10 - 10

-10 - 10 - 10

Loop - 2

$$100 - 10I_2 - 10(I_2 - I_1) - 10(I_2 - I_3) = 0$$

$$100 - 10I_2 - 10I_2 + 10I_1 - 10I_2 + 10I_3 = 0$$

$$100 - 30I_2 + 10I_1 + 10I_3 = 0$$

$$100 = \underline{\underline{-10I_1 + 30I_2 - 10I_3}}$$

$$10 = \underline{\underline{-I_1 + 3I_2 - I_3}} - \textcircled{2}$$

Loop - 3

$$-50 - 10(I_3 - I_2) - 10(I_3 - I_1) = 0$$

$$-50 - 10I_3 + 10I_2 - 10I_3 + 10I_1 = 0$$

$$-50 - 20I_3 + 10I_2 + 10I_1 = 0$$

$$-50 = -10I_1 - 10I_2 + 20I_3$$

$$-5 = -I_1 - I_2 + 2I_3 \quad - \textcircled{3}$$

$$\begin{bmatrix} 0 \\ 10 \\ -5 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 3 & -1 & -1 & 3 & -1 \\ -1 & 3 & -1 & -1 & 3 \\ -1 & -1 & 2 & -1 & 1 \end{vmatrix}$$

$$\Delta = (18 - 1 - 1) - (0 \cdot 3 + 3 + 2) \\ = (16) - 8 = \underline{\underline{8}}$$

$$\Delta_1 = \begin{bmatrix} 0 & -1 & -1 \\ 10 & 3 & -1 \\ -5 & -1 & 2 \end{bmatrix} = \begin{bmatrix} 0 & -1 & -1 & 0 & -1 \\ 10 & 3 & -1 & 10 & 3 \\ -5 & -1 & 2 & -5 & -1 \end{bmatrix}$$

$$= (0 - 5 + 10) - (15 + 0 - 20) \\ = 5 + 5 = \underline{\underline{10}}$$

$$\Delta_2 = \begin{bmatrix} 3 & 0 & -1 \\ -1 & 10 & -1 \end{bmatrix} = \begin{bmatrix} 3 & 0 & -1 & 3 & 0 \\ -1 & 10 & -1 & -1 & 10 \\ -1 & -5 & 2 & -1 & -5 \end{bmatrix}$$

$$= (60+0-5) - (10+15+0)$$

$$= 55 - 25 = \cancel{25} \underline{\underline{30}}$$

$$\Delta_3 = \begin{bmatrix} 3 & -1 & 0 \\ -1 & 3 & 10 \\ -1 & -1 & -5 \end{bmatrix} = \begin{bmatrix} 3 & -1 & 0 & 3 & -1 \\ -1 & 3 & 10 & -1 & 3 \\ -1 & -1 & -5 & -1 & -1 \end{bmatrix}$$

$\cancel{3(-15+10)} + 1(5+10) \quad \cancel{-5+15=0}$

$$= (-45+10+0) - (0-30-5) = -\cancel{35} - \cancel{35}$$

$$= -35 + 35 = 0 \parallel$$



$$I_1 = \frac{\Delta_1}{\Delta} = \frac{10}{8} = 1.25 \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{30}{8} = 3.75 \text{ A}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{0}{8} = 0 \text{ A}$$

~~Three-phase systems~~

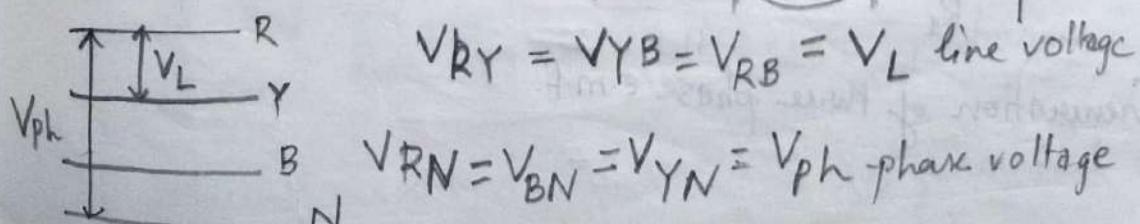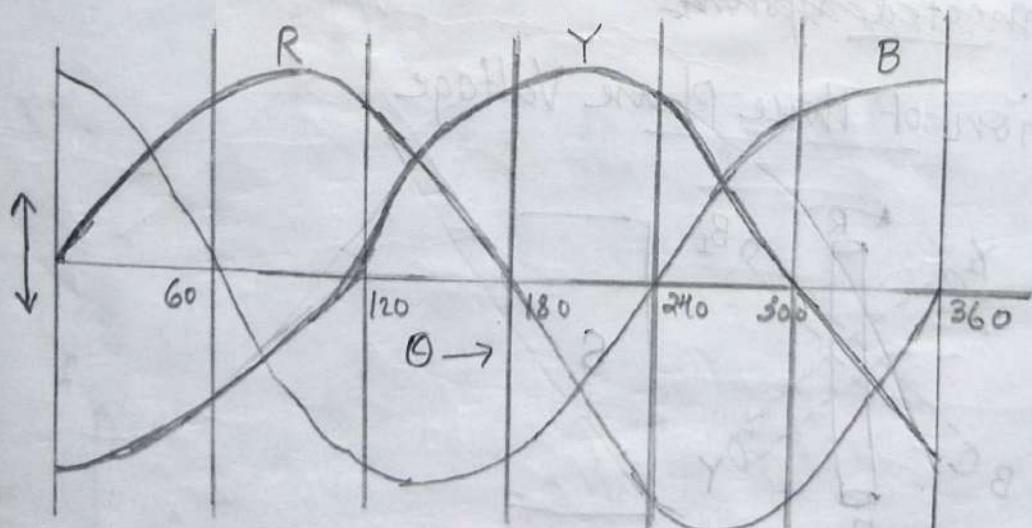~~GECP~~ WAVEFORMS OF THREE PHASE VOLTAGES



The voltage across any one winding is called phase voltage (V_{ph}) (polyphase system)


Advantages of three phase system over single-phase system

- Generation of polyphase power is cheaper.
- Three phase machines has higher efficiency and higher power factor compared to a single phase system.
- For the same size, the output of a polyphase machine is greater than that of a single phase machine, hence it is lighter and cheaper.
- Single phase motors are not self-starting whereas polyphase motors are self starting.
- The parallel operation of single phase alternator is not very smooth whereas three phase alternators run in parallel without any difficulty.

~~Connections of three phase systems~~

~~Star connected system~~

Production of Three Phase Voltage

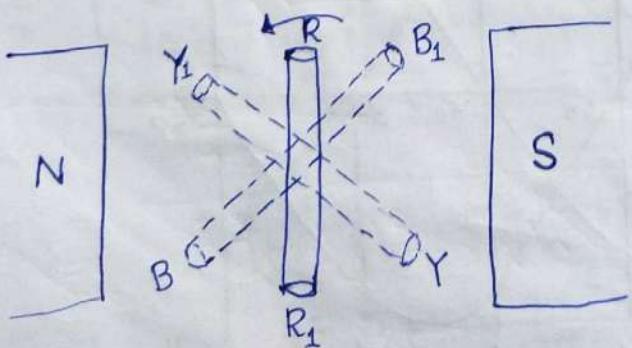

Generation of three phase e.m.f.

- Let ω be the angular velocity in a uniform magnetic field b/w the poles N and S.
- Let R, Y, B be the start terminals and R₁, Y₁, B₁ be the finish terminals of these coils.

Voltage induced in coil RR₁ = V_{RR_1}

Voltage induced in coil YY₁ = V_{YY_1}

Voltage induced in coil BB₁ = V_{BB_1}

When the complete coil system rotates the emf induced in the three coils are all sinusoidal and equal in magnitude.

However, since these coils are displaced 120° in space, the emfs V_{RR_1} , V_{YY_1} and V_{BB_1} also have 120° phase difference.


This system of voltages so obtained are called ~~as~~ 3 phase voltages.

The instantaneous values of generated emfs in coils RR₁ (Phase R), YY₁ (Phase Y) and BB₁ (Phase B) are given by

$$V_{RR_1} = V_m \sin \theta$$

$$V_{YY_1} = V_m \sin(\theta - 120^\circ)$$
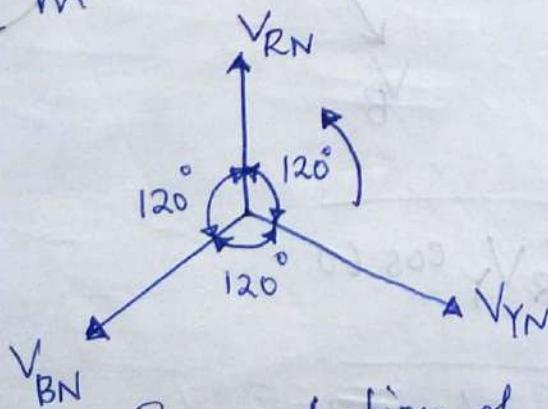
$$V_{BB_1} = V_m \sin(\theta - 240^\circ) \text{ or } V_m \sin(\theta + 120^\circ)$$



Representation of 3 emfs by phasors


where V_m is the maximum value of generated emf in each

of the coils and θ is the position of the coil RR_1 from its initial position.

Phase sequence

- The order in which the phase voltage of three phase system attain their peak or maximum positive value is called the phase sequence of the system.
- When the voltage of the red phase is at its positive maximum value, the voltage of the Y phase will be 120° behind its positive maximum value and that of B phase 240° behind its positive maximum value.
- The phase sequence of the voltages is RYB and the phases are assumed to rotate in an anti-clockwise direction.

Connections of three phase systems

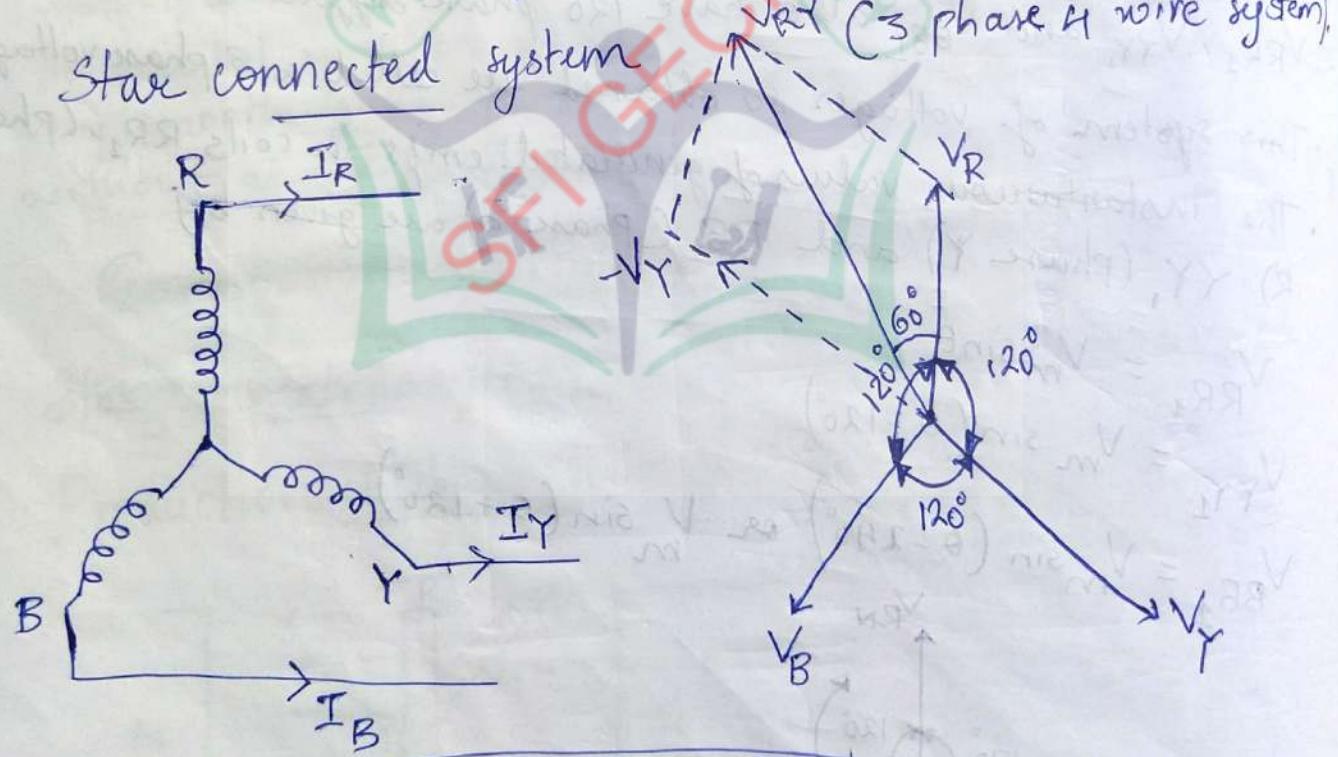

$$V_{RY} = \sqrt{(V_R)^2 + (V_Y)^2 + 2V_R V_Y \cos 60^\circ}$$

$$V_L = \sqrt{V_{ph}^2 + (-V_{ph})^2 + 2V_{ph} V_{ph}}$$

$$V_L = \sqrt{3V_{ph}^2}$$

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

Power in Star Connected system

$P = 3 \times \text{Per phase Power}$

$$3 \times V_{ph} I_{ph} \cos \phi = \sqrt{3} \times \sqrt{3} \times V_{ph} I_{ph} \cos \phi$$


$$P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Active power } P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Reactive power } Q = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Apparent power } S = \sqrt{3} V_L I_L$$

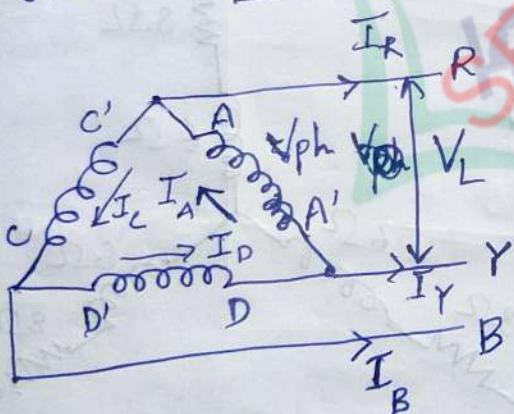Delta Connected system (3 phase 3 wire system)




$$I_R = I_A - I_C$$

$$I_Y = I_D - I_A$$

$$I_B = I_C - I_D$$

$$I_R = \sqrt{I_A^2 + (I_C)^2 + 2 \times I_A \times I_C \cos 60^\circ}$$
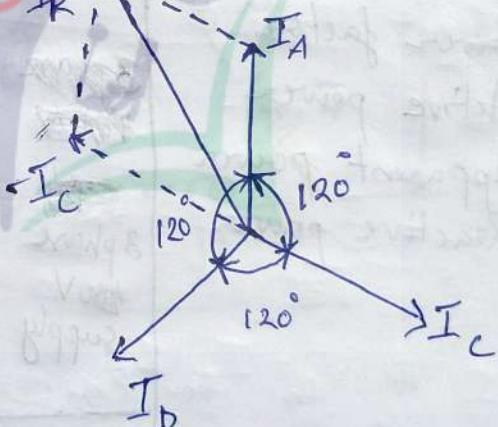
$$= \sqrt{I_{ph}^2 + I_{ph}^2 + I_{ph}^2} \rightarrow \begin{cases} I_L = \sqrt{3} I_{ph} \\ V_L = V_{ph} \end{cases}$$



Power in Delta connected system

$$P = 3 \text{ per phase power}$$

$$= 3 V_{ph} I_{ph} \cos \theta$$

$$= \sqrt{3} \times \sqrt{3} V_{ph} I_{ph} \cos \theta$$

$$P = \sqrt{3} \times V_L I_L \cos \theta$$

$$Q = \sqrt{3} \times V_L I_L \sin \theta$$

$$S = \sqrt{3} V_L I_L$$

A balanced Δ connected load of $(8 + j6)$ Ω per phase is connected to a Δ phase supply 400V . Find



(i)

(ii) Power factor

(iii) Active power

(iv) Apparent power

(v) Reactive power

Impedance per phase, $Z_{ph} = (8 + j6)$

Line voltage $V_L = 400\text{V}$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 \text{ V} = \underline{\underline{231 \text{ V}}}$$

$$|Z_{ph}| = \sqrt{8^2 + 6^2} = 10\Omega$$

Phase current $I_{ph} = V_{ph}/Z_{ph} = 230.94/10 = 23.094 A$

$$I_{ph} = I_L$$

$$\text{i) } I_L = \underline{\underline{23.094 A}}$$

$$\text{ii) Power factor, } \cos \phi = (R/Z) = \underline{\underline{8/10}} = 0.8$$

$$\text{iii) } P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 23.094 \times 0.8 = 12799.9 W = 12.799 kW$$

$$\text{iv) } S = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} \times 400 \times 23.094 = \underline{\underline{15999.9 VA}} = 16 kVA$$

$$\text{v) } Q = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} \times 400 \times 23.094 \times 0.6$$

$$= \underline{\underline{9599.9 VAR}} = \underline{\underline{9.6 kVAR}}$$

* 3 impedances of $4+j3$ are connected in delta & find connected across a 3 phase 400V supply. Find

(i) Line current

(ii) Power factor

(iii) Active power

$$V_L = \frac{V_{ph}}{\sqrt{3}} = \frac{400}{\sqrt{3}} = \frac{400}{1.732} = 230.94 V$$



Ans: $V_L = 400V$

$$V_{ph} = 400V$$

$$|Z_{ph}| = \sqrt{4^2 + 3^2} = \underline{\underline{5\Omega}}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{5} = \underline{\underline{80 A}}$$

$$(i) I_L = \sqrt{3} \times 80 = \underline{\underline{138.56 A}}$$

$$\text{ii) } \text{PF, } \cos\theta = \frac{R/Z}{\sqrt{3}} = \frac{0.8}{\sqrt{3}}$$

$$\text{iii) } P = \sqrt{3} V_L I_L \cos\phi = \sqrt{3} \times 400 \times 138.56 \times 0.8 \\ = 76794.7 \text{ W}$$

$$= 76.794 \text{ kW}$$

- Q.11 P45
P.T.O.
- 3) A three phase delta connected balanced load where connected 400 V supply when connected to draws 17.32 A at 0.8 power factor lagging. Each phase has a resistor and an inductor connecting in series. Find the resistance and reactance per phase.

$$V_L = 400 \text{ V}$$

$$V_{ph} = 400 \text{ V}$$

$$I_L = 17.32 \text{ A}$$

$$\Leftrightarrow \text{P.F. cos}\theta = R/Z = 0.8$$

$$I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{17.32}{\sqrt{3}} = 10 \text{ A}$$

$$\therefore V_{ph} = I_{ph} Z_{ph}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{400}{10} = 40 \Omega$$

$$\cos\theta = R/Z$$

$$R = \sqrt{R^2 + X_L^2} = \sqrt{4^2 + 8^2} = \sqrt{16 + 64} = \sqrt{80} = 8.94 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + X_L^2} = \sqrt{4^2 + 8^2} = \sqrt{16 + 64} = \sqrt{80} = 8.94 \Omega$$

$$X_L = \sqrt{Z^2 - R^2}$$

$$X_L = \sqrt{40^2 - 32^2} = 24 \Omega$$

- (H) Three impedances each having resistance 20Ω and an inductive reactance of 15Ω are connected in star system. AC supply, 3 phase, $400V$. Calculate (i) line current (ii) power factor (iii) total power.

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$V_L = 400V$$

$$|Z_{ph}| = \sqrt{R^2 + X_L^2} = \sqrt{20^2 + 15^2} = 25 \Omega$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$$

$$\begin{aligned} \text{SF} \\ \text{SF} \\ \text{GEO} \end{aligned}$$


$$I_{ph} = V_{ph} / Z_{ph} = \frac{231}{25} = 9.24 A$$

$$I_L = \frac{9.24 A}{\sqrt{3}} = 5.12 A$$

$$(i) \cos \theta = R/Z = \frac{20}{25} = 0.8$$

$$(ii) P = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} \times 400 \times 9.24 \times 0.8 = 5.12 \text{ kW}$$

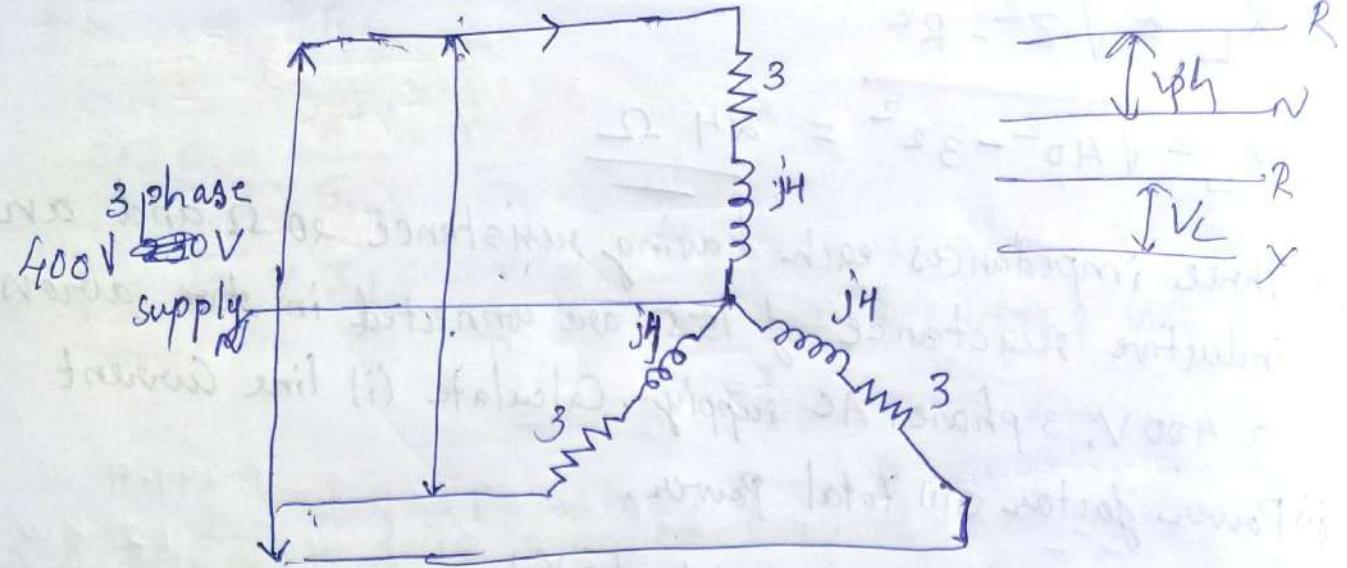- (iii) Find the line current, power factor and the total power for the given star circuit.



$$V_{ph} = \cancel{400V} 230V$$

$$Z = 3 + j4$$

$$V_L = \sqrt{3} V_{ph}$$

$$I_L = I_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 132.8V \quad V_L = \sqrt{3} \times 230 = 398.37V$$

$$|Z_{ph}| = \sqrt{3^2 + 4^2} = \cancel{5 \Omega}$$

$$I_L = 46A$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230}{\cancel{5}} = \cancel{46A}$$

$$\cos \theta = \frac{R}{Z} = \frac{3}{5} = \underline{\underline{0.6}}$$

$$P = \sqrt{3} V_L I_L \cos \theta = \sqrt{3} \times 398.37 \times 46 \times 0.6 = 19.04 kW$$

- (b) A star connected 3 phase load consist of 3 identical impedances. When the load is connected to a 3 phase, 400V supply the line current is 23.09A and PF is 0.8 lagging. Calculate the total power taken by the load? If the load were reconnected in delta and supplied from the same 3 phase supply, calculate the current flow in each line.

$$V_L = 400 V$$

$$V_L = \sqrt{3} V_{ph}$$

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 V$$

$$I_L = I_{ph}$$

$$\boxed{\Delta} I_L = 23.09 A$$

$$I_{ph} = 23.09 A$$

$$V_{ph} = I_{ph} \times Z_{ph} \quad P = \sqrt{3} V_L I_L \cos \theta$$

$$= \sqrt{3} \times 400 \times 23.09 \times 0.8$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{231}{23.09} = \cancel{12.79} = 12.79 \text{ KW}$$

$$V_L = 400 V$$

$$V_{ph} = \underline{400 V}$$

$$Z_{ph} = 10.004 \Omega$$

$$\boxed{\Delta} I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{400}{10.004} = 39.98 A$$

$$I_L = \sqrt{3} \times 39.98 = \underline{\underline{69.24 A}}$$

$$V_L \cancel{V_{ph}}$$

$$V_{ph} = I_{ph} \times Z_{ph}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{231}{23.09} = \underline{\underline{10.004 \Omega}}$$

Admittance

Admittance is the reciprocal of impedance and is denoted by Y . For an AC circuit Admittance, $Y = \frac{1}{Z} = \frac{1}{R + jX}$

$$= \frac{\text{RMS } I}{\text{RMS } V}$$


If the impedance is represented by $R+jX$ then the admittance can be found as follows.

$$\text{Admittance, } Y = \frac{1}{Z} = \frac{1}{R+jX} = \frac{R-jX}{(R+jX)(R-jX)} = \frac{R-jX}{R^2+X^2}$$

$$= R - j \frac{\phi}{R^2 + X^2} \frac{X}{R^2 + X^2}$$

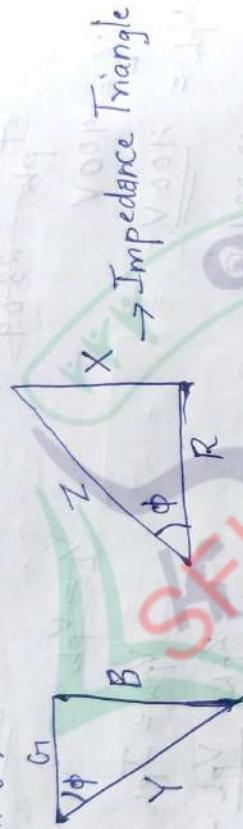
- 1) Conductance (G) given by $\frac{R}{R^2 + X^2}$
 2) Susceptance (B) given by $\frac{X}{R^2 + X^2}$

Unit for admittance, conductance and susceptance is
 Siemens (S) ohm⁻¹ mho.



AC Fundamentals

Figure - 1

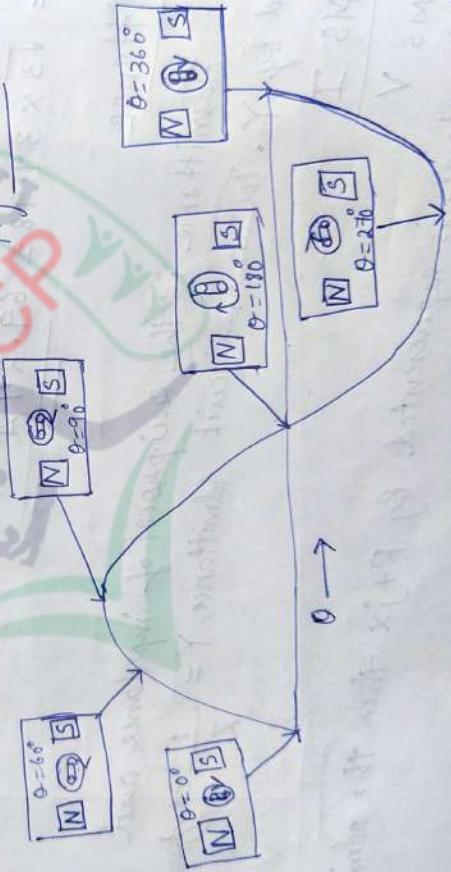

Relation b/w the coil position and induced voltage.

Figure -2


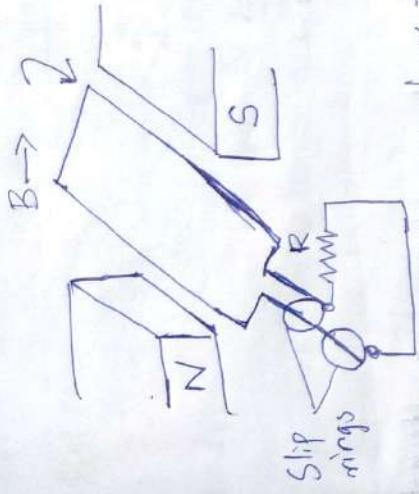


Figure 1 shows a single turn coil placed in a magnetic field, the coil is rotated in an axis \perp to the direction of magnetic field and the ends of the coil are connected to two slip rings when the coil is rotated an emf is induced in the coil with magnitude proportional to the magnetic field, length of coil with speed of cutting the magnetic field. As the coil rotates in the magnetic field, the voltage induced in the conductor and speed of cutting the magnetic field, the voltage induced in the coil is given by $e = V_m \sin \theta$. Here the voltage induced in the coil is given by $e = V_m \sin \theta$. When the coil rotates parallel to the field ($\theta = 90^\circ$) the induced voltage is zero. As θ increases from 0° to 90° , the induced voltage increases and reaches the maximum value when $\theta = 90^\circ$. From 90° to 180° , the induced voltage reduces as shown in fig. From 180° to 360° , the induced voltage will be -ve and the negative peak occurs at 270° . At 360° , the coil reaches in its position and the cycle is repeated.

Considering the angular speed of the coil as ω radians, the induced voltage is given by the equation $V = V_m \sin \omega t$, where V_m peak value of induced emf.

Angular speed $\omega = 2\pi f$

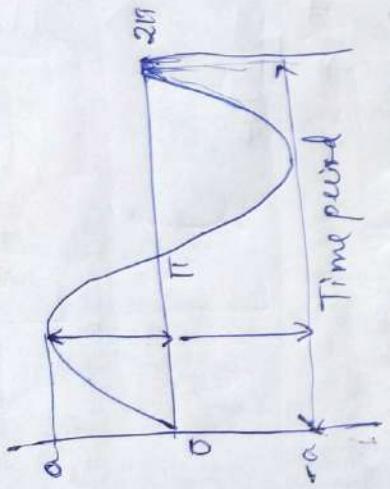

Cycle

One complete set of +ve and -ve values of an alternating quantity is called a cycle.

Periodic Time

The time taken for one cycle is known as time period or periodic time.

$$T = \frac{1}{f}$$

Amplitude

It is the magnitude of the maximum +ve or negative value of alternating quantity.

Frequency

The no. of cycles completed in one second is called frequency of alternating quantity. It is expressed in cycles/second or Hertz.

Instantaneous value

The value of V or I at a particular instant is

wave is the arithmetic mean of the ordinates at equal intervals over a half cycle of the wave.

Root Mean Square value (R.M.S) value

RMS value of an alternating quantity may be defined as the dc current which when flows through a given resistance produces the same amount of heat as that produced by the alternating current passing through the same resistance for the same time. RMS value is also called the effective value.

ing



$$V_{\text{R.M.S}} = \sqrt{V_1^2 + V_2^2 + V_0^2}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} (1 - \cos 2\omega t) d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left[\int_0^{2\pi} 1 d\omega t - \int_0^{2\pi} \cos 2\omega t d\omega t \right]}$$

~~STICKER~~

~~GURU~~

~~CEP~~

$$= \sqrt{\frac{V_m^2}{4\pi} \left[\int_0^{2\pi} (V_m \sin \omega t - \frac{V_m \sin 2\omega t}{2})^2 dt \right]}$$

$$V_{rms} = \sqrt{\frac{V_m^2 \times \pi}{2}}$$

$$= \sqrt{\frac{V_m^2}{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

1) Find the rms value for a half wave rectifier circuit.



$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 dt}$$

$$= \sqrt{\frac{1}{2\pi} \left[V_m^2 \int_0^{2\pi} \sin^2 \omega t d\omega t + C \right]}$$

$$= \sqrt{\frac{1}{2\pi} \left[\int_0^T V_m^2 (1 - \cos 2\omega t) dt \right]}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \int_0^T (1 - \cos 2\omega t) d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left[\omega t - \sin 2\omega t \right]_0^{\frac{\pi}{2}}}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left[\frac{\pi - \sin \pi}{2} - \left(0 - \sin 0 \right) \right]}$$

$$= \sqrt{\frac{V_m^2 \times \pi}{4\pi}}$$

$$= \sqrt{\frac{V_m^2 \times \pi}{4\pi}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\text{Average} = \frac{1}{T} \int_0^T V_{rms} dt$$

alternating
current find the

i) For a half wave rectified sinusoidal current following.

(i) v.m.s value.

(ii) Average value.

$$\text{Ans: (i) } I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \omega t dt}$$

$$= \sqrt{\frac{1}{2\pi} \left[\frac{I_m^2}{2} \sin^2 \omega t \right]_0^{2\pi}}$$

$$I_{avg} = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t dt$$

$$= \sqrt{\frac{1}{2\pi} \times I_m^2 \int_0^{\pi} \sin^2 \omega t dt}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} dt \left[\omega t - \frac{\cos 2\omega t}{2} \right]}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\pi - \frac{\sin 2\pi}{2} - (0) \right]}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \times \pi} = \frac{I_m}{2\sqrt{\pi}}$$

$$(ii) I_{avg} = \frac{1}{2\pi} \int_0^{\pi} I_m \sin \omega t dt$$

$$= \frac{I_m}{2\pi} \int_0^{\pi} \sin \omega t d\omega t$$

$$= \frac{I_m}{2\pi} \left[-\cos \omega t \right]_0^{\pi} = \frac{I_m}{2\pi} \left[-\cos \pi + \cos 0 \right]$$

$$= \frac{I_m}{2\pi} \times 2 = \frac{I_m}{\pi}$$

-1+1


(2) Determine the form factor for the saw tooth wave form
for the so

Let K be the slope of the portion OA. The instantaneous value of the wave form can be written as

$$V = Kt$$

$$K = \frac{E_m}{T}$$

$$V = \frac{E_m}{T} t$$

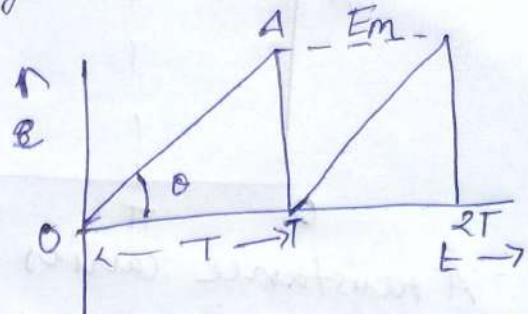

$$\text{# } V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

Form factor = $\frac{\text{RMS value}}{\text{Average value}}$

$$E_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{E_m t}{T}\right)^2 dt}$$

$$= \sqrt{\frac{1}{T^3} \times \int_0^T E_m^2 t^2 dt} = \sqrt{\frac{E_m^2}{T^3} \left[\frac{t^3}{3}\right]_0^T}$$

$$= \sqrt{\frac{E_m^2}{T^3} \left[\frac{T^3}{3}\right]}$$

$$= \sqrt{\frac{E_m^2}{T^8} \times \frac{T^3}{3}} = \frac{E_m}{\sqrt{3}}$$


$$E_{\text{avg}} = \frac{1}{T} \int_0^T \frac{E_m}{T} t dt$$

$$= \frac{E_m}{T^2} \left[\frac{t^2}{2}\right]_0^T = \frac{E_m}{2}$$

$$\text{Form factor} = \frac{\frac{E_m}{\sqrt{3}} \times 2}{E_m} = \frac{2}{\sqrt{3}}$$

$$= \frac{2}{\sqrt{3}}$$

(3)

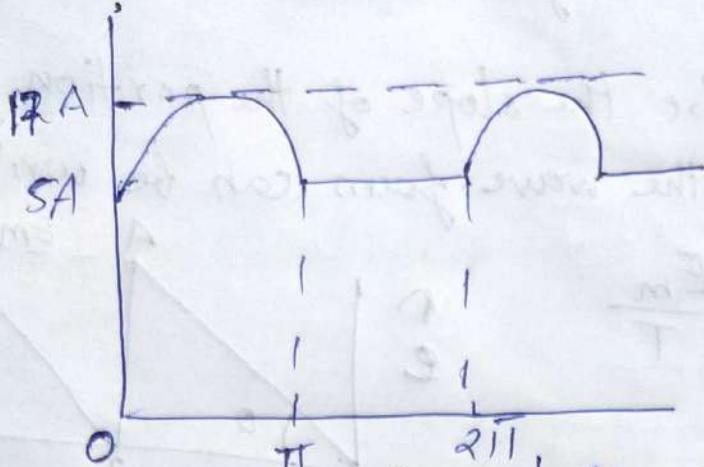

A resistance carries a half rectified sinusoidal current of peak value 12 A superimpose on a dc. of 5 A. Determine the average and r.m.s values of the total current.

$$I_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} (5 + 12 \sin \omega t)^2 d\omega t + \int_{\pi}^{2\pi} 5^2 d\omega t}$$

$$\bar{I}_{\text{avg}} = \frac{1}{2\pi} \left(\int_0^{\pi} (5 + 12 \sin \omega t) d\omega t + \int_{\pi}^{2\pi} 5 d\omega t \right)$$