



# സഹായി

SFI GEC PALAKKAD

8-08-19  
Thursday

# Active and Passive elements

Active elements - supply


Transistor


Passive elements - Receive

Resistor, Inductor, Capacitor

store and dissipate

Resistor  $\rightarrow R$   Unit ohm  $\Omega$

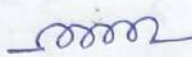Inductor  $\rightarrow L$   Henry H

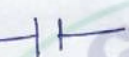Capacitor  $\rightarrow C$   Farad F


Current Flow  $\rightarrow$  +ve to -ve  
Higher potential to lower

Voltage rise  $\rightarrow$  -ve to +ve

Voltage drop  $\rightarrow$  +ve to -ve



Resistors in Series

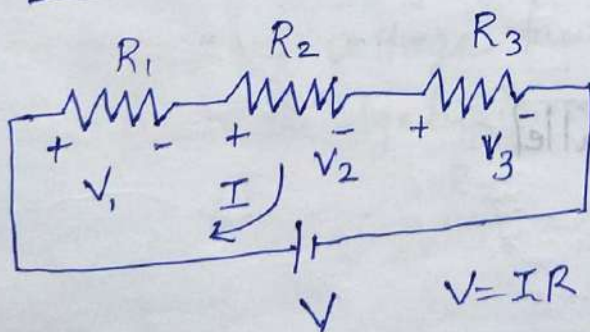

$$V - V_1 - V_2 - V_3 = 0$$

$$V - IR_1 - IR_2 - IR_3 = 0$$


$$V - I(R_1 + R_2 + R_3) = 0$$

$$V = I(R_1 + R_2 + R_3)$$

$$V = IR_{\text{equivalent}}$$

$$I = \frac{V}{R_{\text{equivalent}}}$$

Resistor in Series

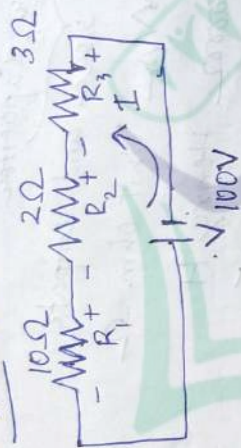

$$R_{eq} = R_1 + R_2 + R_3 = 10\Omega + 2\Omega + 3\Omega = 15\Omega$$

$$V = 100V$$


$$I = V/R$$

$$I = \frac{100}{15} = 6.66 A$$

Current will always flow from higher potential to lower potential

$$\text{So, } I = 6.66 A$$

Resistor in Parallel

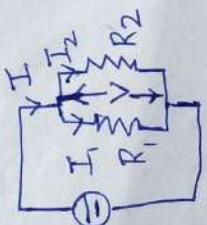

$$I = I_1 + I_2$$

$$I = \frac{V}{R_1} + \frac{V}{R_2}$$




$$I = V \left[ \frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$I = V \left[ \frac{R_1 + R_2}{R_1 R_2} \right]$$

$$V = I \left[ \frac{R_1 R_2}{R_1 + R_2} \right]$$

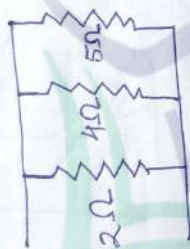7 Determine the total resistance for the following network.



$$R_1 = 2\Omega$$

$$R_2 = 4\Omega$$

$$R_3 = 5\Omega$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R} = \frac{1}{2} + \frac{1}{4} + \frac{1}{5} = 0.95$$


$$R = \frac{1}{0.95} = 1.053 \Omega$$

14-08-2019

Kirchoff's laws

Kirchoff's Voltage law (KVL)

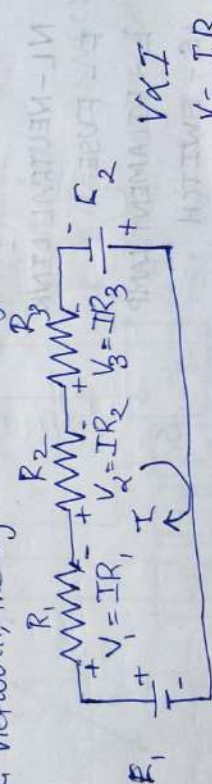Kirchoff's voltage law states that for any closed path in a network, the algebraic sum of all the voltages is zero.



$$E_1 - V_1 - V_2 - V_3 + E_2 = 0$$

$$E_1 + E_2 = V_1 + V_2 + V_3$$

$$E_1 + E_2 = I (R_1 + R_2 + R_3)$$


$$V = IR$$

## Kirchoff's Current Law (KCL)

Current law states that at the junction of circuit elements the algebraic sum of all the currents will be equal to zero.

Current law states that sum of currents entering a junction is equal to sum of the current leaving the junction.

Eg:

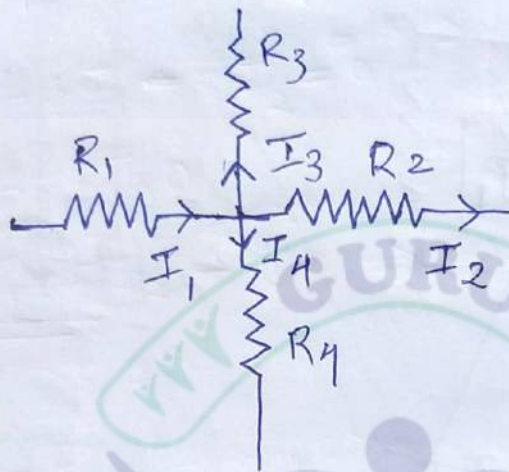


$$I_1 = I_3 + I_4 + I_2$$

For the following circuit,

1) determine  $V_2$  Using KVL

2) Determine  $I$

3) Find  $R_1$  and  $R_3$

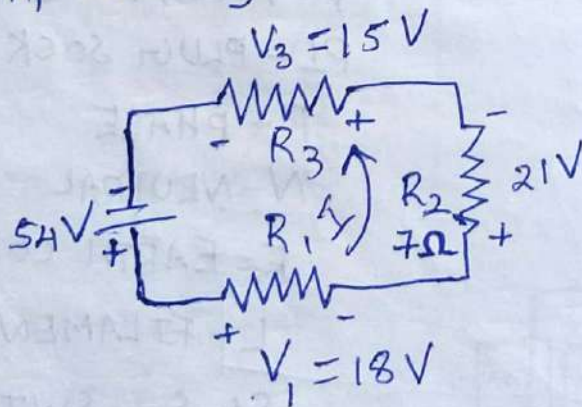

$$1) E_1 + E_2 = I(R_1 + R_2 + R_3)$$

$$E_1 = 54V$$



$$54 = 18V + V_2 + 15V$$

$$54V = 33V + V_2$$

$$V_2 = 54 - 33 = \underline{\underline{21V}}$$



2)  $V_1 = IR_1$   $V_1 = 18V$   $R_2 = 7\Omega$   
 $V_2 = 21V$

$$V_2 = IR_2$$

$$21 = I \times 7$$

$$7I = 21$$

$$I = \frac{21}{7} = \underline{\underline{3A}}$$

(3)  $V_1 = IR_1$

$$V_1 = 18V$$

$$I = 3$$

$$18 = R_1 = \frac{V_1}{I}$$

$$R_1 = \frac{18}{3} = \underline{\underline{6\Omega}}$$


$$V_3 = IR_3$$

$$I = 3A$$

$$V_3 = 15V$$

$$R_3 = \frac{V_3}{I} = \frac{15}{3} = \underline{\underline{5\Omega}}$$

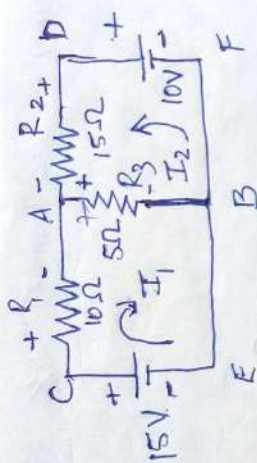? For the following circuit find the currents in the resistors  $R_1$ ,  $R_2$  and  $R_3$ .



$$I_1 = I(R_1 + R_2)$$

loop 1

$$15 - 10I_1 - 5I_1 + 5I_2 = 0 \Rightarrow 15 - 15I_1 + 5I_2 = 0$$

$$15 - 10I_1 - 5I_1 + 5I_2 = 0$$

$$15 - 15I_1 + 5I_2 = 0$$

$$15 = 15I_1 - 5I_2 \Rightarrow 3 = 3I_1 - I_2 \quad (1)$$

loop 2

$$10 - I_2 - 15I_2 - 5(I_2 + I_1) = 0$$

$$10 - 15I_2 - 5I_2 - 5I_1 = 0$$

$$10 - 20I_2 - 5I_1 = 0$$

$$10 = 20I_2 + 5I_1 \Rightarrow 2 = 4I_2 + I_1 \quad (2)$$

$$3I_1 + I_2 = 3$$

$$4I_2 + I_1 = 2$$

$$3I_1 + I_2 = 3$$

$$-3I_1 + 12I_2 = 6$$

$$-11I_2 = -3$$

$$I_2 = \frac{-3}{-11} = \frac{3}{11}$$


$$3I_1 + 3 = 3$$

$$3I_1 = 3 - 3 = 0$$

$$I_1 = \frac{0}{11} = 0$$



1. Find the current in the following circuit find the current in resistors  $R_1, R_2, R_3$ .

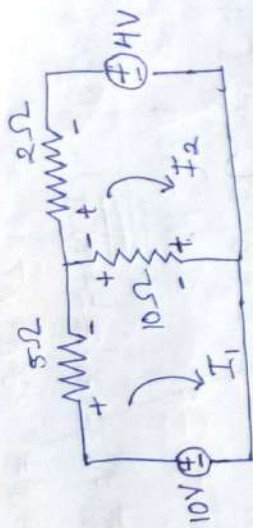

loop 1

$$10 - 5I_1 - 10(I_1 - I_2) = 0$$

$$10 - 5I_1 - 10I_1 + 10I_2 = 0$$

$$10 - 15I_1 + 10I_2 = 0$$

$$10 = 15I_1 - 10I_2 \quad \text{--- (1)}$$

loop 2

$$-4 - 10(I_2 - I_1) - 2I_2 = 0$$

$$-4 - 10I_2 + 10I_1 - 2I_2 = 0$$

$$-4 - 12I_2 + 10I_1 = 0$$

$$-4 = 12I_2 - 10I_1 \quad \text{--- (2)}$$

$$15I_1 - 10I_2 = 10$$

$$-10I_1 + 12I_2 = -4$$

$$\begin{array}{r} 5I_1 \quad 15I_1 - 10I_2 = 10 \\ + \quad -10I_1 + 12I_2 = -4 \\ \hline 5I_1 - 10I_2 = 10 \\ 0 + 8I_2 = 4 \end{array}$$

$$I_2 = \frac{4}{8} = \frac{1}{2} = 0.5 \text{ A}$$



$$3I_1 - 2 \times \frac{1}{2} = 2$$

$$3I_1 - 1 = 2$$

$$3I_1 = 2 + 1 = 3$$

$$I_1 = 1 \text{ A}$$

$$5(I_1 - I_2) = 0$$


$$5(1 - I_2) = 0$$

$$5 \times \frac{2-1}{2} = 0$$

$$5 \times \frac{1}{2} = 0$$

$$I_1 - I_2 = \frac{5}{2} \text{ A}$$

Mesh Analysis

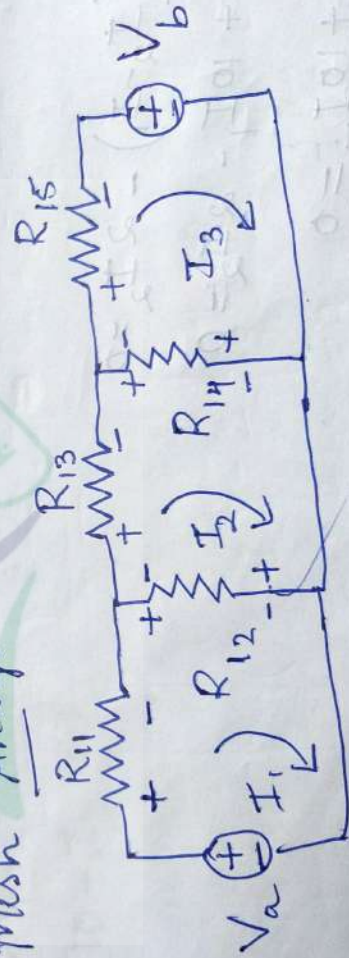

Loop 1

$$V_a - I_1 R_{11} - I_1 R_{12} - (I_1 - I_2) R_{13} = 0$$

Loop 1

$$V_a - I_1 R_{11} - R_{12} (I_1 - I_2) = 0$$

$$V_a - I_1 R_{11} - I_1 R_{12} + I_2 R_{12} = 0$$

$$V_a - I_1 (R_{11} + R_{12}) + I_2 R_{12} = 0$$

$$V_a = I_1 (R_{11} + R_{12}) - I_2 R_{12} \quad \text{--- ①}$$

Loop 2

$$-R_{12} (I_2 - I_1) - I_2 R_{13} - R_{14} (I_2 - I_3) = 0$$

$$-R_{12} I_2 + R_{12} I_1 - I_2 R_{13} - R_{14} I_2 + R_{14} I_3 = 0$$

$$-I_2 (R_{12} + R_{13} + R_{14}) + R_{12} I_1 + R_{14} I_3 = 0$$

$$I_2 (R_{12} + R_{13} + R_{14}) - R_{12} I_1 - R_{14} I_3 = 0 \quad \text{--- ②}$$

Loop 3

$$-V_b - R_{14} (I_3 - I_2) - I_3 R_{15} = 0$$

$$-V_b - R_{14} I_3 + R_{14} I_2 - I_3 R_{15} = 0$$

$$-V_b - I_3 (R_{14} + R_{15}) + R_{14} I_2 = 0$$

$$-V_b = I_3 (R_{14} + R_{15}) - R_{14} I_2 \quad \text{--- ③}$$

This equation can be put in a matrix form as

$$\begin{bmatrix} V_a \\ 0 \\ -V_b \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} R_{11} + R_{12} & -R_{12} & 0 \\ -R_{12} & R_{12} + R_{13} + R_{14} & -R_{14} \\ 0 & -R_{14} & R_{14} + R_{15} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$



By Applying Cramer's rule,


$$\text{determinant } \Delta = \begin{vmatrix} R_{11}+R_{12} & -R_{12} & 0 \\ -R_{12} & R_{12}+R_{13}+R_{14} & -R_{14} \\ 0 & -R_{14} & R_{14}+R_{15} \end{vmatrix}$$

$$\Delta_1 = \begin{vmatrix} V_a & -R_{12} & 0 \\ 0 & R_{12}+R_{13}+R_{14} & -R_{14} \\ -V_b & -R_{14} & R_{14}+R_{15} \end{vmatrix}$$

$$\Delta_2 = \begin{vmatrix} R_{11}+R_{12} & V_a & 0 \\ -R_{12} & 0 & -R_{14} \\ 0 & -V_b & R_{14}+R_{15} \end{vmatrix}$$

$$\Delta_3 = \begin{vmatrix} R_{11}+R_{12} & -R_{12} & V_a \\ -R_{12} & R_{12}+R_{13}+R_{14} & 0 \\ 0 & -R_{14} & -V_b \end{vmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta}, I_2 = \frac{\Delta_2}{\Delta}, I_3 = \frac{\Delta_3}{\Delta}$$

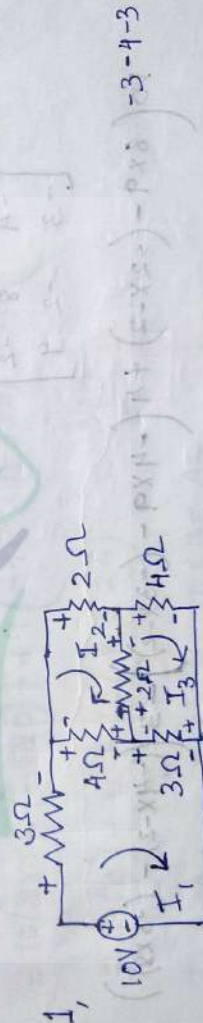

Loop 1

$$10 - 3I_1 - 4(I_1 - I_2) - 3(I_1 - I_3) = 0$$

$$10 - 3I_1 - 4I_1 + 4I_2 - 3I_1 + 3I_3 = 0$$

$$10 - 10I_1 + 4I_2 + 3I_3 = 0 \quad 10 = 10I_1 - 4I_2 - 3I_3$$

Loop-2

$$-2I_2 - 2(I_2 - I_3) - 4(I_2 - I_1) = 0 \quad -2-2-4$$

$$-2I_2 - 2I_2 + 2I_3 - 4I_2 + 4I_1 = 0$$

$$-8I_2 + 2I_3 + 4I_1 = 0$$

$$8I_2 - 2I_3 - 4I_1 = 0 \quad -\textcircled{2}$$

Loop-3

$$-2(I_3 - I_2) - 4I_3 - 3(I_3 - I_1) = 0$$

$$-2I_3 + 2I_2 - 4I_3 - 3I_3 + 3I_1 = 0$$

$$-9I_3 + 2I_2 + 3I_1 = 0$$

$$9I_3 - 2I_2 - 3I_1 = 0$$

$$\begin{bmatrix} 10 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

$$\begin{bmatrix} 10 & -4 & -3 \\ -4 & 8 & -2 \\ -3 & -2 & 9 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 10 & -4 & -3 \\ -4 & 8 & -2 \\ -3 & -2 & 9 \end{bmatrix}$$

$$10(8 \times 9 - (-2 \times -2)) + 4(-4 \times 9 - (-3 \times -2)) - 3((-4 \times -2) - (-3 \times 8))$$

$$10(72 - 4) + 4(-36 - 6) - 3(8 + 24)$$

$$680 - 168 - 96 = \underline{\underline{416}}$$

A



$$\Delta_1 = \begin{bmatrix} 10 & -4 & -3 \\ 0 & 8 & -2 \\ 0 & -2 & 9 \end{bmatrix}$$

$$\Delta_1 = 10(8 \times 9 - (-2 \times -2)) + 4(0 \times 9 - (0 \times -2)) - 3(0 \times -2 - (0 \times 8))$$

$$= 10(72 - 4) + 4(0) - 3(0) = \underline{\underline{680}}$$

$$\Delta_2 = \begin{bmatrix} 10 & 10 & -3 \\ -4 & 0 & -2 \\ -3 & 0 & 9 \end{bmatrix}$$

$$= 10(0 \times 9 - (0 \times -2)) - 10(-4 \times 9 - (-3 \times -2)) + 3(-4 \times 0 - (-3 \times 0))$$

$$= 10(0) - 10(-36 - 6) + 3(0)$$

$$= \underline{\underline{420}}$$

$$\Delta_3 = \begin{bmatrix} 10 & -4 & 10 \\ -4 & 8 & 0 \\ -3 & -2 & 0 \end{bmatrix}$$

$$= 10(8 \times 0 - (-2 \times 0)) + 4(-4 \times 0 - (-3 \times 0)) + 10(-4 \times -2 - (-3 \times 8))$$


$$= 10(0) + 0 + 10(8 + 24) = \underline{\underline{320}}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{680}{416} = \underline{\underline{1.635 \text{ A}}}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{420}{416} = \underline{\underline{1.0096 \text{ A}}}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{320}{416} = \underline{\underline{0.769 \text{ A}}}$$

3,

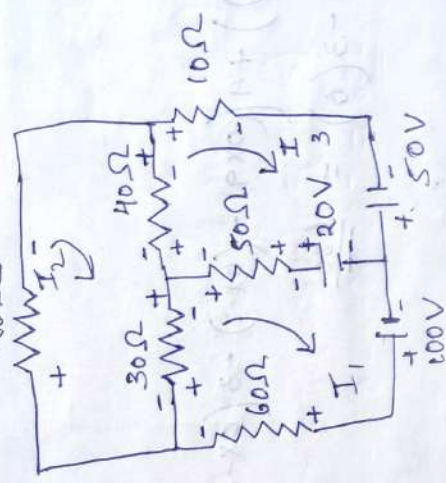

Loop 1

$$100 - 60I_1 - 30(I_1 - I_2) - 50(I_1 - I_3) = 0$$

$$100 - 60I_1 - 30I_1 + 30I_2 - 50I_1 + 50I_3 = 0 \quad \times 0 \quad - 60I_1 + 30I_2 - 50I_3 = 0$$

$$100 - 140I_1 + 30I_2 + 50I_3 = 0$$

$$100 = 140I_1 - 30I_2 - 50I_3 \quad \text{--- (1)}$$

Loop 2

$$-20I_2 - 40(I_2 - I_3) = 0$$

$$-20I_2 - 40I_2 + 40I_3 = 0 \quad \times 0 \quad -20I_2 - 40I_2 + 40I_3 = 0$$

$$-60I_2 + 40I_3 = 0$$

$$-60I_2 + 40I_3 = 0 \quad \times 3 \quad -180I_2 + 120I_3 = 0$$

$$8 = 14I_1$$

Loop 2

$$-20I_2 - 40(I_2 - I_3) - 30(I_2 - I_1) = 0$$

$$-20I_2 - 40I_2 + 40I_3 - 30I_2 + 30I_1 = 0$$

$$-90I_2 + 40I_3 + 30I_1 = 0$$



$$90I_2 - 40I_3 - 30I_1 = 0 \quad (2)$$

loop-3

$$50 + 20 - 50(I_3 - I_1) - 40(I_3 - I_2) - 10I_3 = 0$$

$$70 - 50I_3 + 50I_1 - 40I_3 + 40I_2 - 10I_3 = 0$$

$$70 - 100I_3 + 50I_1 + 40I_2 = 0$$

$$70 = 100I_3 - 50I_1 - 40I_2 \quad (3)$$

$$\begin{bmatrix} 80 \\ 0 \\ 70 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 140 & 30 & 50 \\ -30 & -90 & -40 \\ -50 & 40 & 100 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 140 & 30 & 50 \\ -30 & -90 & -40 \\ -50 & 40 & 100 \end{bmatrix}$$

$$= 140(-90 \times 100 - (40 \times -40))$$

$$- 30(-30 \times 100 - (-50 \times -40)) - 50(-30 \times 40 - (-50 \times -90))$$

$$= -30(-3000 - 2000) - 50(-1200 - 4500) + 140(-9000 + 1600)$$

$$= -30 \times -5000 - 50 \times -5700 + 140(-7400)$$

$$= 150000 + 285000 - 285000$$

$$\begin{bmatrix} 80 \\ 0 \\ 70 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 140 & 30 & 50 \\ -30 & -90 & -40 \\ -50 & 40 & 100 \end{bmatrix}$$

$$\begin{bmatrix} 8 \\ 0 \\ 7 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 14 & 3 & 5 \\ -3 & 9 & -4 \\ -5 & 4 & 10 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 14 & -3 & -5 \\ -3 & 9 & -4 \\ -5 & -4 & 10 \end{bmatrix}$$

$$= 14((-3)(-4) - (-5)(-4)) + 3((-3)(10) - (-5)(-4)) - 5((-3)(-4) - (-5)(-4))$$

$$= 14(90 - 16) + 3(-30 - 20) - 5(12 + 45)$$

$$= 1036 - 150 - 270 = 285 = \underline{\underline{601}}$$

$$\Delta_1 = \begin{bmatrix} 8 & -3 & -5 \\ 0 & 9 & -4 \\ 7 & -4 & 10 \end{bmatrix}$$

$$= 8((9)(10) - (-4)(-4)) + 3((0)(10) - (7)(-4)) - 5((0)(-4) - (7)(9))$$

$$= 8(90 - 16) + 3(0 + 28) - 5(0 - 63)$$

$$= 592 + 84 + 315 = 991 = \underline{\underline{991}}$$

$$\Delta_2 = \begin{bmatrix} 14 & 8 & -5 \\ -3 & 0 & -4 \\ -5 & 7 & 10 \end{bmatrix}$$

$$= 14((0)(10) - (-4)(-4)) - 8((-3)(10) - (-5)(-4)) - 5((-3)(7) - (-4)(-5))$$

$$= 14(0 - 16) - 8(-30 - 20) - 5(-21 - 20)$$

$$= 392 + 400 + 105 = 897 = \underline{\underline{897}}$$

$$\Delta_3 = \begin{bmatrix} 14 & -3 & 8 \\ -3 & 9 & 0 \\ -5 & -4 & 7 \end{bmatrix}$$

$$= 14((-3)(7) - (-4)(0)) + 3((-3)(7) - (-5)(0)) + 8((-3)(-4) - (-5)(9))$$

$$= 14(-21) + 3(-21) - 8(12 + 45) = 882 - 63 + 456 = 1275$$



$$I_1 = \frac{\Delta_1}{\Delta} = \frac{991}{601} = \underline{\underline{1.64 \text{ A}}}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{897}{601} = \underline{\underline{1.49 \text{ A}}}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{363}{601} = \underline{\underline{0.60 \text{ A}}}$$

Determine the power dissipated in all the three resistors in the following figure using Mesh current Analysis.



Loop 1

$$-10 + 8 - 50 - 200(I_1 - I_2) + 8 - 50I_1 = 0$$

$$-2 - 200I_1 + 200I_2 - 50I_1 = 0$$

$$-2 - 250I_1 + 200I_2 = 0$$

$$-2 = 250I_1 - 200I_2 \quad \text{--- (1)}$$

Loop 2

$$40 - 200(I_2 - I_1) + 10 - 100I_2 = 0$$

$$50 - 200I_2 + 200I_1 - 100I_2 = 0$$

$$50 - 300I_2 + 200I_1 = 0$$

$$50 = 300I_2 - 200I_1 \quad \text{--- (2)}$$

$$1 = 6I_2 - 4I_1$$

$$P = V \cdot I$$

$$V = IR$$

$$P = I^2 R$$

$$125I_1 - 100I_2 = -1$$

$$-4I_1 + 6I_2 = 1$$

$$-500I_1 + 400I_2 = 4$$

$$-500I_1 + 750I_2 = 125$$

$$0 + -350I_2 = -121$$

$$I_2 = \frac{-121}{-350} = 0.34 \text{ A}$$

$$-4I_1 + 6 \times 0.34 = 1$$

$$-4I_1 + 2.04 = 1$$

$$-4I_1 = 1 - 2.04 = -1.04$$

$$I_1 = \frac{+1.04}{+4} = 0.26 \text{ A}$$

$$\text{Power dissipated in } 50 \Omega \text{ resistor} = I^2 R$$

$$= (0.26)^2 \times 50 = 3.38 \text{ W}$$

$$\text{Power dissipated in } 100 \Omega \text{ resistor} = I_1^2 R$$


$$= (0.34)^2 \times 100 = 11.56 \text{ W}$$

$$\text{Power dissipated in } 200 \Omega \text{ resistor} = (I_2 - I_1)^2 R$$

$$= 1.28 \text{ W}$$



# Node Analysis

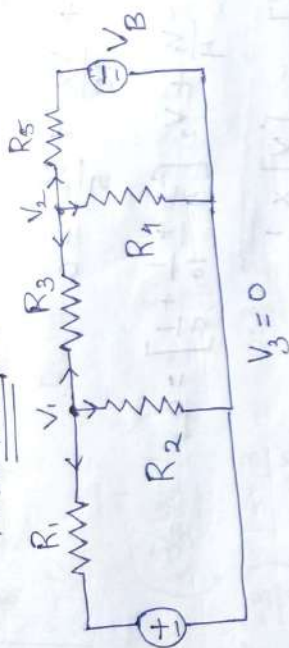

$$V_3 = 0$$

Node 1


$$V_1 - V_A + \frac{V_1}{R_1} + \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$

$$V_1 \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{V_2}{R_3} = \frac{V_A}{R_1}$$

Node 2

$$\frac{V_2 - V_1}{R_3} + \frac{V_2}{R_4} + \frac{V_2 - V_B}{R_5} = 0$$
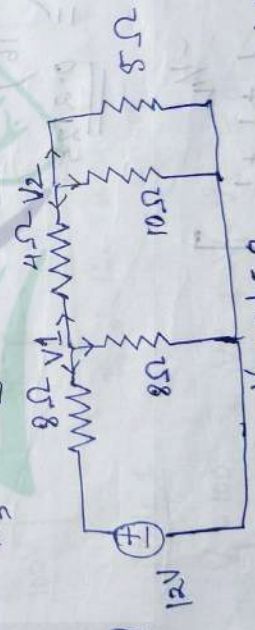
$$-\frac{V_1}{R_3} + V_2 \left[ \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right] = \frac{V_B}{R_5}$$



$$V_{ground} = 0$$

Find the current through  $5\Omega$  resistor using node analysis.

Node 1

$$\frac{V_1 - 12}{8} + \frac{V_1}{8} + \frac{V_1 - V_2}{10} = 0$$

$$V_1 \left[ \frac{1}{8} + \frac{1}{8} + \frac{1}{10} \right] - \frac{V_2}{10} = \frac{12}{8}$$

Node - 2

$$\frac{V_2 - V_1}{4} + \frac{V_2}{10} + \frac{V_2}{5} = 0$$

$$V_2 \left( \frac{1}{4} + \frac{1}{10} + \frac{1}{5} \right) - \frac{V_1}{4} = 0$$

$$[I] = \frac{[V]}{[R]}$$

$$\begin{bmatrix} 12 \\ 8 \\ 0 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \begin{bmatrix} \frac{1}{8} + \frac{1}{4} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{10} + \frac{1}{5} \end{bmatrix}$$

$$\Delta = \begin{bmatrix} \frac{1}{8} + \frac{1}{4} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{4} + \frac{1}{10} + \frac{1}{5} \end{bmatrix}$$

$$\frac{1}{8} + \frac{1}{4} + \frac{1}{4} \times \frac{1}{4} + \frac{1}{10} + \frac{1}{5} - \left( -\frac{1}{4} \times -\frac{1}{4} \right)$$

$$= 0.5 \times 0.55 - \left( \frac{1}{16} \right)$$

$$= 0.275 - 0.0625 = 0.2125$$

$$A_1 = \begin{bmatrix} \frac{3}{2} & -\frac{1}{4} \\ 0 & \frac{1}{4} + \frac{1}{10} + \frac{1}{5} \end{bmatrix}$$

$$\frac{3}{2} \times \frac{1}{4} + \frac{1}{10} + \frac{1}{5} - \left( 0 \times -\frac{1}{4} \right) = 0.825$$



$$\Delta_2 = \begin{bmatrix} \frac{1}{8} + \frac{1}{8} + \frac{1}{4} & 3/2 \\ -1/4 & 0 \end{bmatrix}$$

$$= 0 - \left( \frac{3}{2} \times -\frac{1}{4} \right)$$


$$= - \left( \frac{-3}{8} \right) = \frac{3}{8} = \underline{\underline{0.375}}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{0.825}{0.2125} \quad V_1 = \frac{\Delta_1}{\Delta} = \frac{0.825}{0.2125} = \underline{\underline{3.88 V}}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{0.375}{0.2125} = \underline{\underline{1.76 V}}$$

$$I_2 = \frac{V_2}{5}$$
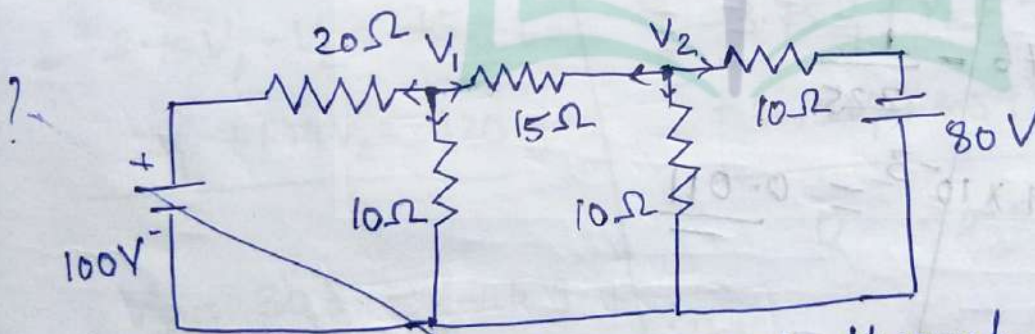
$$I_2 = \frac{1.76}{5} = \underline{\underline{0.352 A}}$$




Find the current through 15Ω Resistor

Node 1

$$\frac{V_1 - 100}{20} + \frac{V_1}{10} + \frac{V_1 - V_2}{15} = 0$$
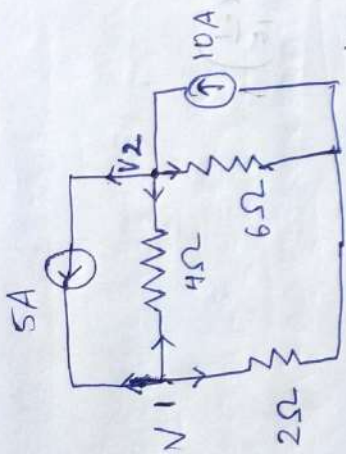
$$V_1 \left( \frac{1}{20} + \frac{1}{10} + \frac{1}{15} \right) - \frac{V_2}{15} = \frac{100}{20} \quad \text{--- ①}$$



Find the node voltage in the following circuit.

Node 1

$$\frac{V_1}{2} + \frac{V_1 - V_2}{4} - 5 = 0$$

$$V_1 \left[ \frac{1}{2} + \frac{1}{4} \right] - \frac{V_2}{4} = 5 \quad \text{--- (1)}$$

Node-2

$$\frac{V_2}{6} + \frac{V_2 - V_1}{4} - 10 + 5 = 0$$

$$-\frac{V_1}{4} + V_2 \left( \frac{1}{6} + \frac{1}{4} \right) = 5 \quad \text{--- (2)}$$

$$V_1 \cdot 0.75 - \frac{V_2}{4} = 5 \quad \text{--- (1)}$$

$$3V_1 - V_2 = 20 \quad \text{--- (1)}$$

$$-\frac{V_1}{4} + 0.416 V_2 = 5$$

$$-V_1 + 1.664 V_2 = 20$$

$$3V_1 - V_2 = 20$$

$$-V_1 + 1.664 V_2 = 20$$



$$-3V_1 + V_2 = -20$$

$$-3V_1 + 4.992V_2 = 60$$

$$-20-60$$


$$0 + -3.992V_2 = -80$$

$$V_2 = \frac{-80}{-3.992} = 20.04 \text{ V}$$

$$-3V_1 + 20 = -20$$

$$-3V_1 = -20-20 = -40$$
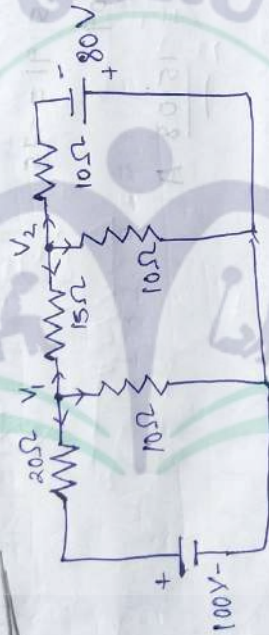
$$V_1 = \frac{-40}{-3} = 13.33 \text{ V}$$



Node-1

$$V_1 - 100 + \frac{V_1}{10} + \frac{V_1 - V_2}{15} = 0$$

$$V_1 \left( \frac{1}{20} + \frac{1}{10} + \frac{1}{15} \right) - \frac{V_2}{15} = \frac{100}{20} \quad \text{--- (1)}$$

Node-2

$$\frac{V_2 - V_1}{15} + \frac{V_2}{10} + \frac{V_2 + 80}{10} = 0$$

$$-\frac{V_1}{15} + V_2 \left( \frac{1}{15} + \frac{1}{10} + \frac{1}{10} \right) = -8 \quad \text{--- (2)}$$

$$-\frac{V_1}{15} + 0.27 V_2 = -8$$

$$-V_1 + 4.05V_2 = -120 \quad \text{--- (2)}$$

$$-V_1 + 405x - 25.91 = -120$$

$$-V_1 - 104.93 = -120$$

$$-V_1 = -120 + 104.93$$

$$-75 + 390.6$$

$$-75 + 25.91$$

$$-12.18 \sqrt{2} = 815.6$$


$$V_a = \frac{315.6}{-12.18} = -25.91 \text{ A}$$

$$-3.255V - 25.91 = -75$$

$$-3.255V_1 = -49.09$$

$$V_1 = \frac{-49.09}{-3.255} = 15.08 \text{ A}$$
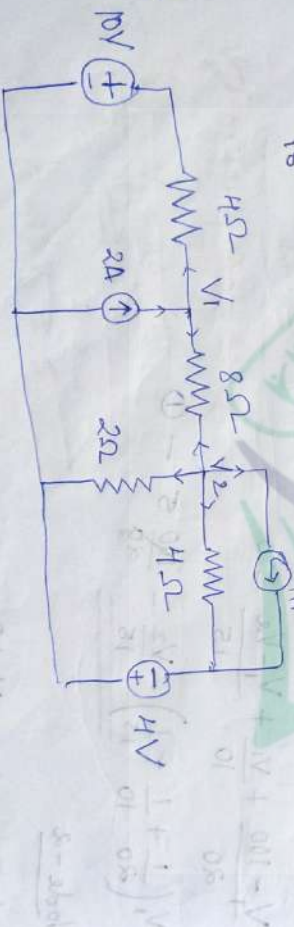
$$I = \frac{V_2 - V_1}{15} = \frac{-25.91 - 15.08}{15} = \underline{\underline{2.73 \text{ A}}}$$



Find the node voltages of the given circuit



Node - 1

$$\frac{V_1 - 10}{4} - 2 + \frac{V_1 - V_2}{8} = 0$$

$$V_1 \left( \frac{1}{4} + \frac{1}{8} \right) - \frac{10}{4} - 2 - \frac{V_2}{8} = 0$$

$$V_1 \left( \frac{1}{4} + \frac{1}{8} \right) - \frac{V_2}{8} = 0 \quad \text{--- ①}$$

Node - 2

$$\frac{V_2}{2} + 4 + \frac{V_2 + 4}{4} = 0$$

$$\frac{V_2 - V_1}{8} + \frac{V_2}{2} + 4 + \frac{V_2 + 4}{4} = 0$$

$$\frac{-V_1}{8} + V_2 \left( \frac{1}{8} + \frac{1}{2} + \frac{1}{4} \right) + 4 + 1 = 0$$

$$\frac{-V_1}{8} + V_2 \left( \frac{1}{8} + \frac{1}{2} + \frac{1}{4} \right) = -5$$

$$0.375V_1 - \frac{V_2}{8} = \frac{9}{2} \quad \text{--- ②}$$

$$\frac{-V_1}{8} + 0.375V_2 = -5 \quad \text{--- ③}$$

$$3V_1 - V_2 = 36 \quad \text{--- ④}$$

$$\frac{-V_1 + 7V_2}{8} = -40 \quad \text{--- ⑤}$$

$$\frac{-3V_1 + 21V_2}{8} = -120$$

$$0 \quad -20V_2 = 84$$

$$V_2 = \frac{84}{-20} = -4.2 \text{ V}$$

$$-3V_1 - 4 \cdot 2 = -36$$


$$-3V_1 = -36 + 4 \cdot 2$$

$$-3V_1 = -31.8$$

$$V_1 = \frac{-31.8}{-3} = 10.6 \text{ V}$$

Star-Delta Conversion

Star

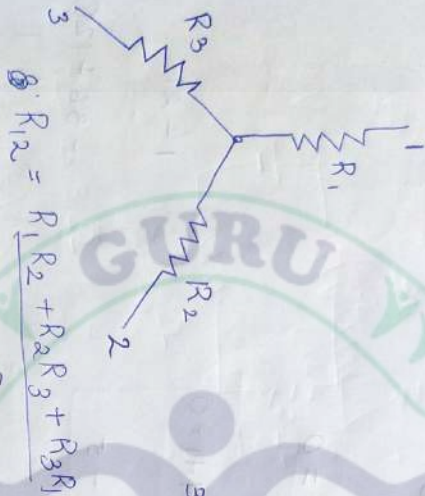

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_{32} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

Delta



Delta-Star Conversion





$$R_1 = \frac{R_{12} \times R_{31}}{R_{12} + R_{32} + R_{31}}$$




$$R_2 = \frac{R_{12} \times R_{32}}{R_{12} + R_{32} + R_{31}}$$

$$R_3 = \frac{R_{31} \times R_{32}}{R_{12} + R_{32} + R_{31}}$$

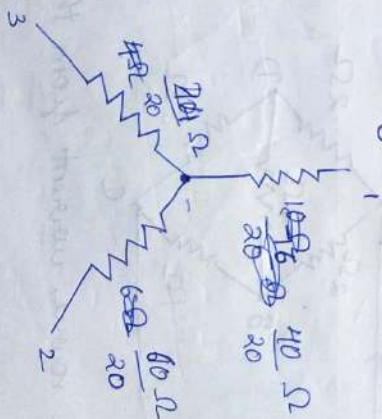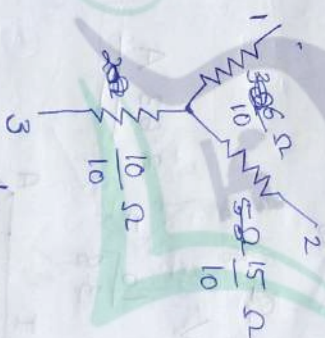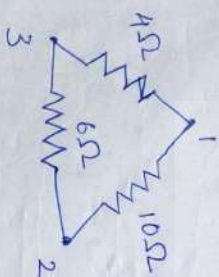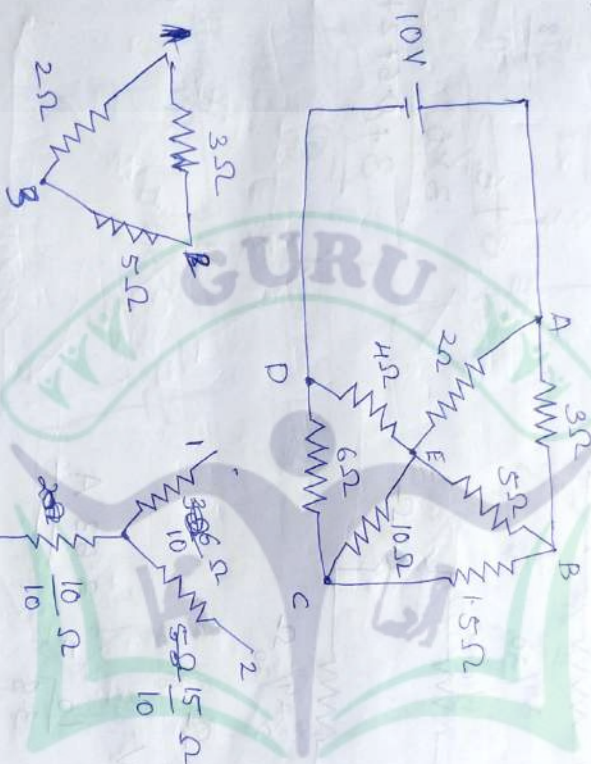Using star-delta transformation, Calculate the I drawn from the battery in the following.




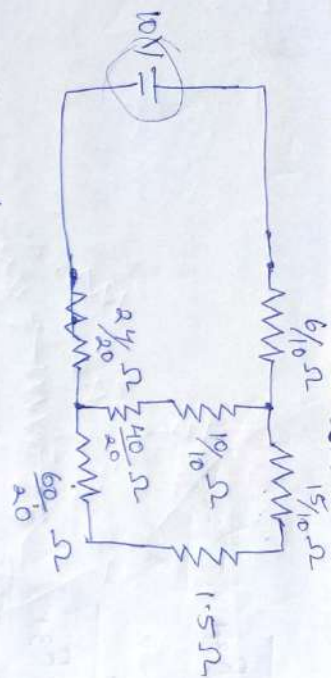

$$4.5 + 1.5 = 6$$



$$= 6$$

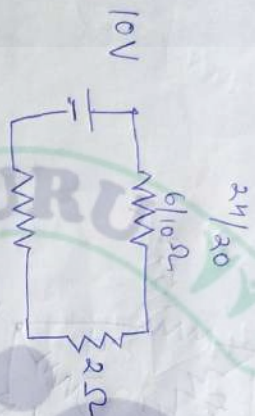


$$\frac{3 \times 6}{3 + 6 + 2 + 1.2} = \frac{18}{9} = 2$$

$$R = 3.8 \Omega$$





$$V = 10 V$$
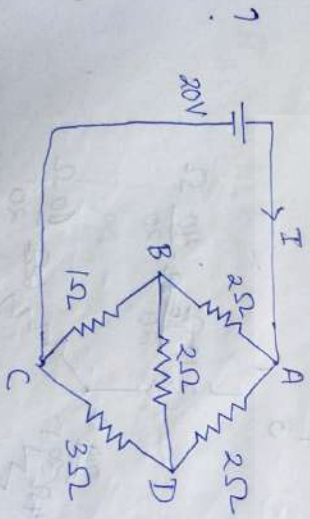
$$I = \frac{V}{R} = \frac{10}{3.8} = 2.63 A$$



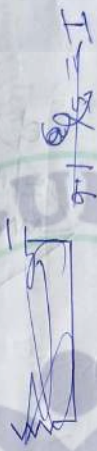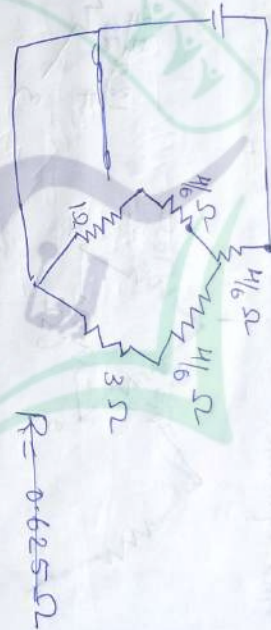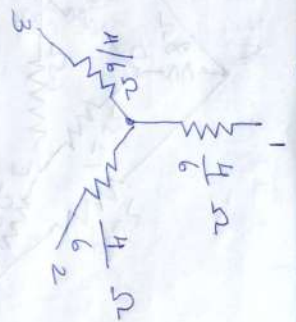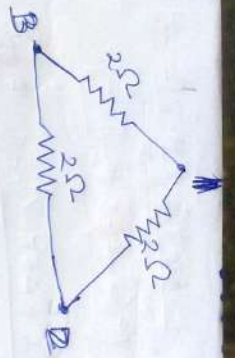Find the current I from the given circuit.






$$I = \frac{V}{R} = \frac{20}{0.625} = 32$$



$$R = 11.45 + \frac{2}{3} = 1.812 \Omega$$

$$I = \frac{V}{R} = \frac{20}{1.812} = 11.03 A$$

8

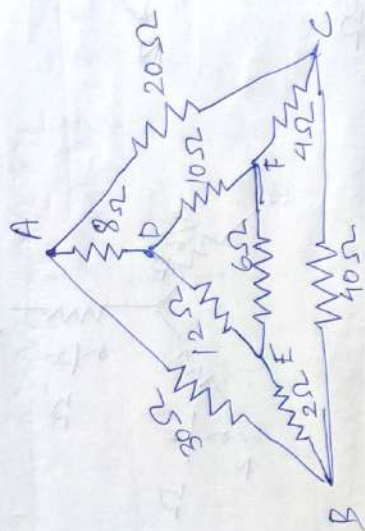

Find equivalent resistance across AB

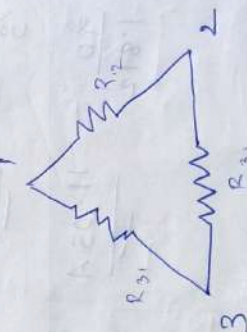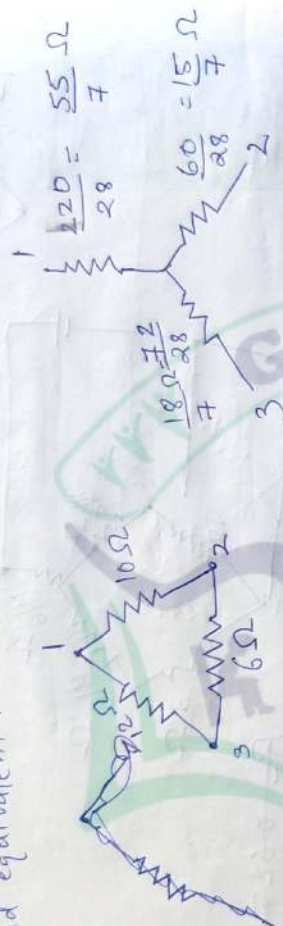

$$R_{12} = \frac{111}{7} + \frac{43}{7} + \frac{32}{7} = \frac{196}{7} = 28 \Omega$$



$$= \frac{97.4 + 28.08 + 72.4}{4.57} = 43.2 \Omega$$


4.57

$$R_{32} = \frac{97.4 + 28.08 + 72.4}{15.85} = 12.18 \Omega$$

15.85

$$R_{13} = \frac{97.4 + 28.08 + 72.4}{6.14} = 32.22 \Omega$$

6.14

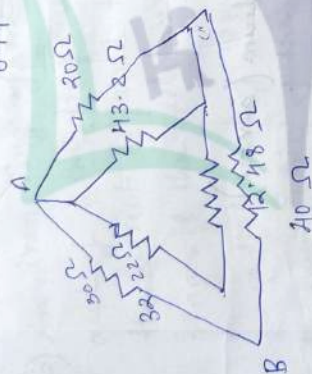

$$\text{Equivalent resistance across } = \frac{30 \times 32.22}{30 + 32.22} = 15.53 \Omega$$